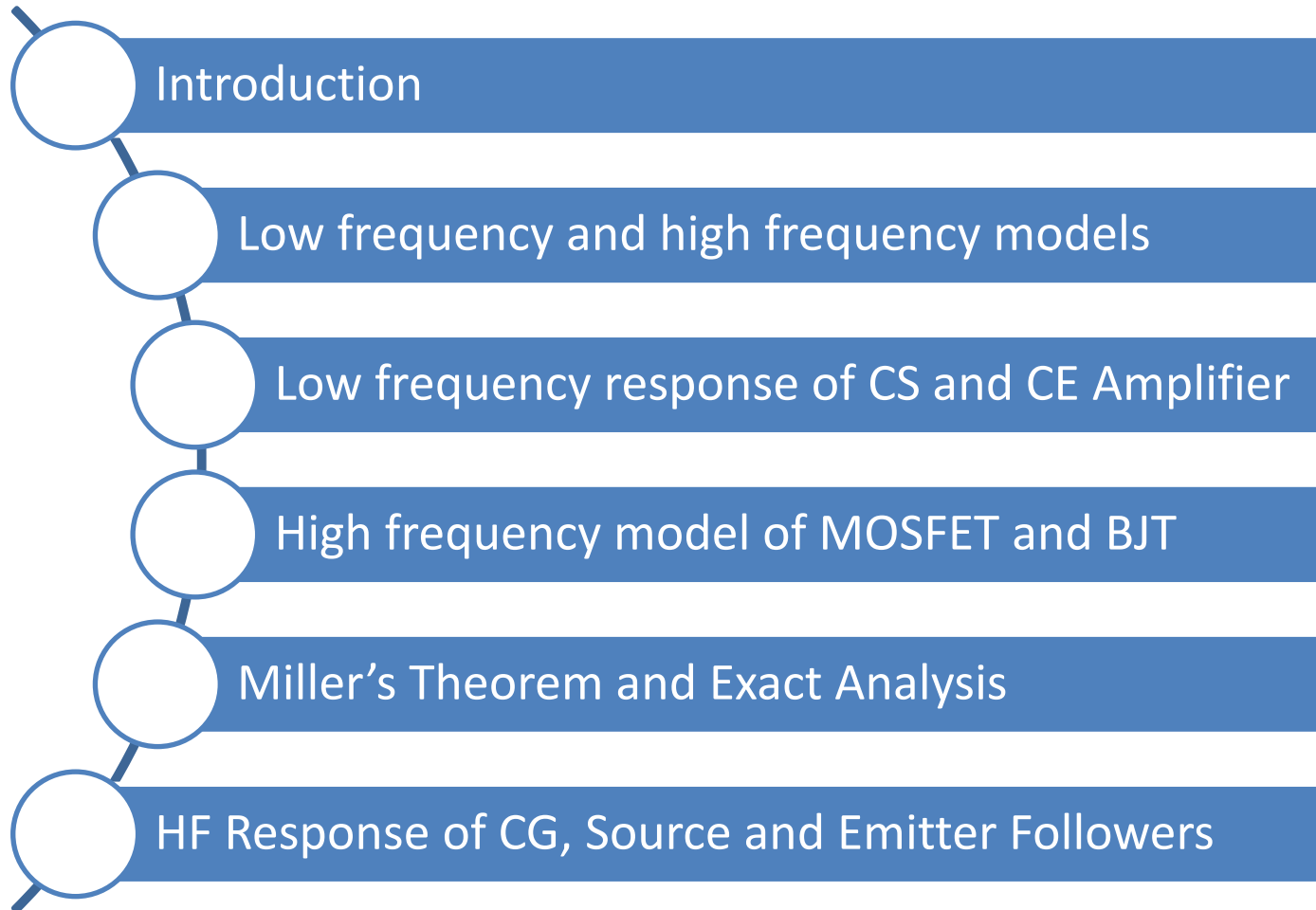


# Electronic Circuits


## Chapter 5: Frequency Response

Dr. Dung Trinh

# Outline





# Introduction

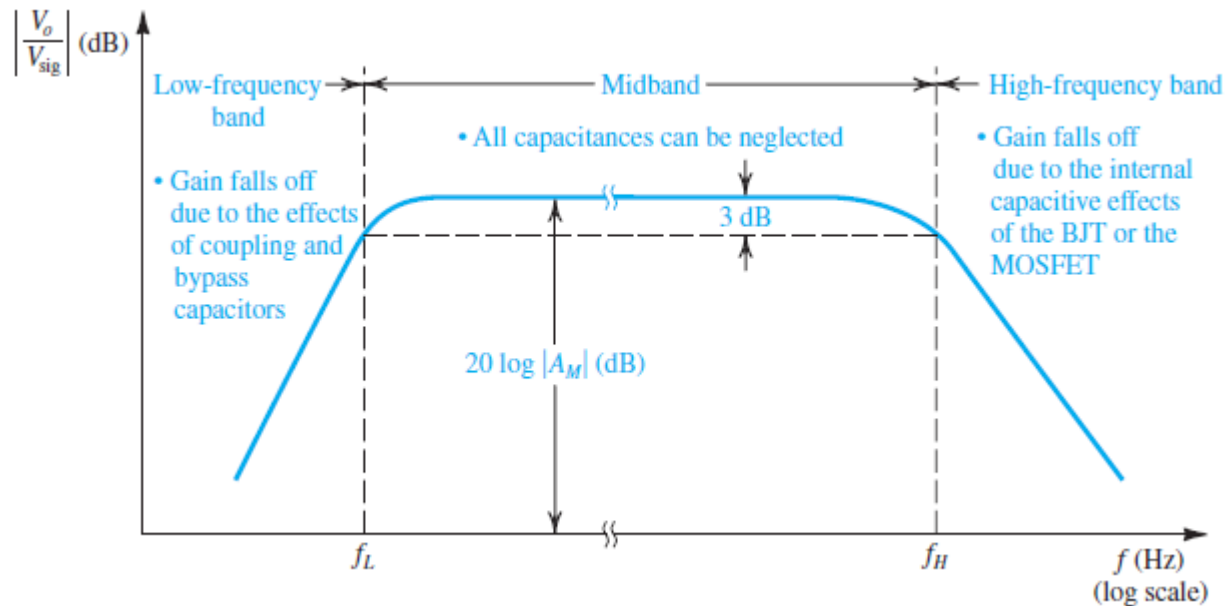

*At lower frequencies*, the magnitude of the amplifier gain falls off. This occurs because the *coupling and bypass capacitors* no longer have low impedances.

The gain of the amplifier falls off at *the high-frequency* end. This is due to internal capacitive effects in the BJT and in the MOSFET.

# Introduction: Low-pass Circuit

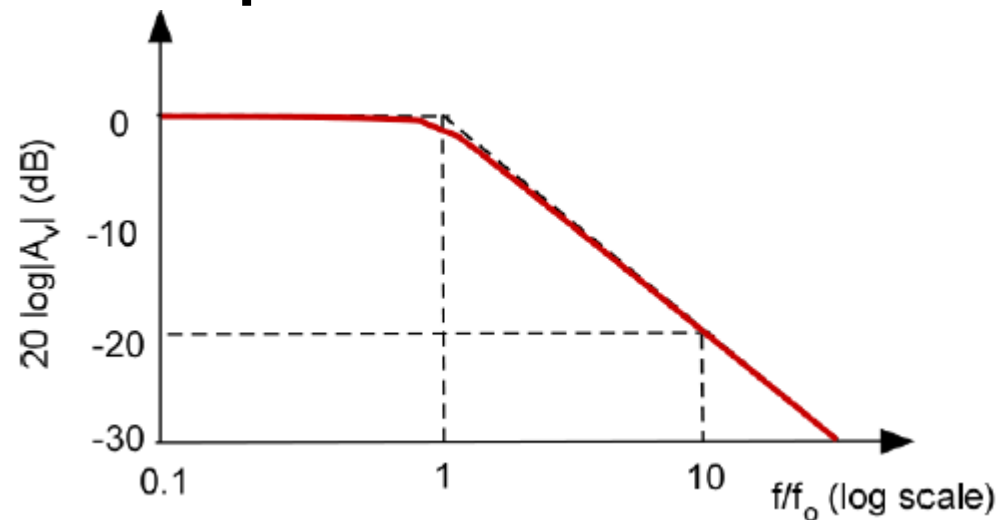
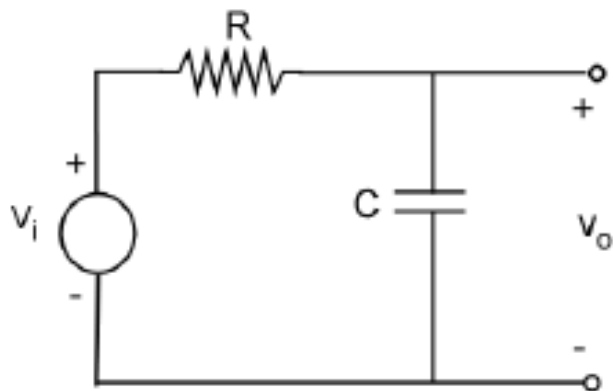


In frequency domain:  $V_o = \frac{V_i}{R + \frac{1}{j\omega C}} \cdot \frac{1}{j\omega C} = \frac{V_i}{1 + j\omega RC}$

$$\rightarrow A_v = \frac{V_o}{V_i} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + jf/f_0}$$

$$f_0 = \frac{1}{2\pi RC} = \frac{1}{\tau} \quad \tau = 2\pi RC$$

# Introduction: High-pass Circuit

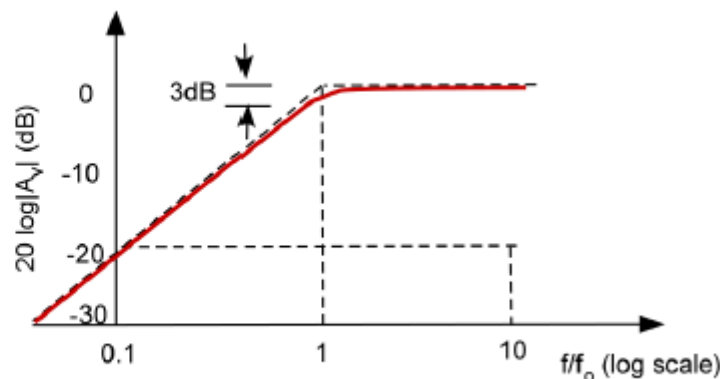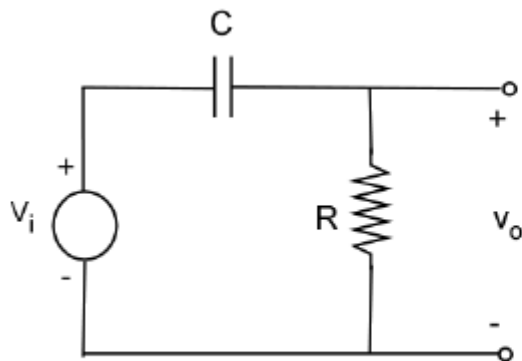

In frequency domain:  $V_o = \frac{V_i R}{R + \frac{1}{j\omega C}} = \frac{V_i}{1 + \frac{1}{j\omega RC}}$

$$\rightarrow A_v = \frac{V_o}{V_i} = \frac{1}{1 - j \frac{1}{\omega RC}} = \frac{1}{1 - j f_0 / f}$$

$$f_0 = \frac{1}{2\pi RC} = \frac{1}{\tau} \quad \tau = 2\pi RC$$

# Introduction: Octave vs Decade

If  $f_2 = 2f_1$ , then  $f_2$  is one octave above  $f_1$ .

If  $f_2 = 10f_1$ , then  $f_2$  is one decade above  $f_1$

$$\# \text{ of octave} = \log_2 \frac{f_2}{f_1} = 3.32 \log_{10} \frac{f_2}{f_1}$$

$$\# \text{ of decade} = \log_{10} \frac{f_2}{f_1}$$

## Example:

2 GHz is one octave above 1 GHz

10 GHz is one decade above 1 GHz

# Introduction: 3dB definition

**3dB points** are points at which the magnitude is  $\frac{1}{\sqrt{2}}$  that at mid-band frequency.

**Power** is halved. Voltage is scaled as:

$$\frac{V_o}{|1 + j|} = \frac{V_o}{\sqrt{2}}$$

*From which:*

$$A_{dB} = 20 \log_{10} (\sqrt{2}) = 3dB$$

# Introduction: Gain

Amplifier has intrinsic gain:  $A_0$

Low-pass characteristics:  $\frac{1}{1+j^f/f_{hi}}$

High-pass characteristics:  $\frac{j^f/f_{lo}}{1+j^f/f_{lo}}$

Overall gain:  $A(f) = A_0 \frac{1}{1+j^f/f_{hi}} \frac{j^f/f_{lo}}{1+j^f/f_{lo}}$

At very high frequency, the gain becomes:

$$G = -20 \log_{10} \sqrt{1 + (\omega/\omega_0)^2} \approx -20 \log_{10} (\omega/\omega_0)$$


Slope of curve is **-20db/decade**


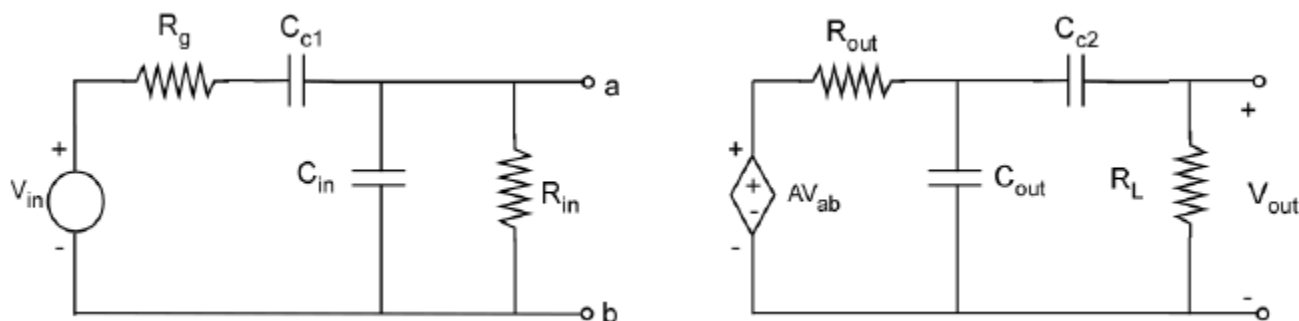
# Model for general amplifying element


$C_{c1}$  and  $C_{c2}$  are coupling capacitors (large):  $\mu F$ .

$C_{in}$  and  $C_{out}$  are parasitic capacitors (small):  $pF$ .



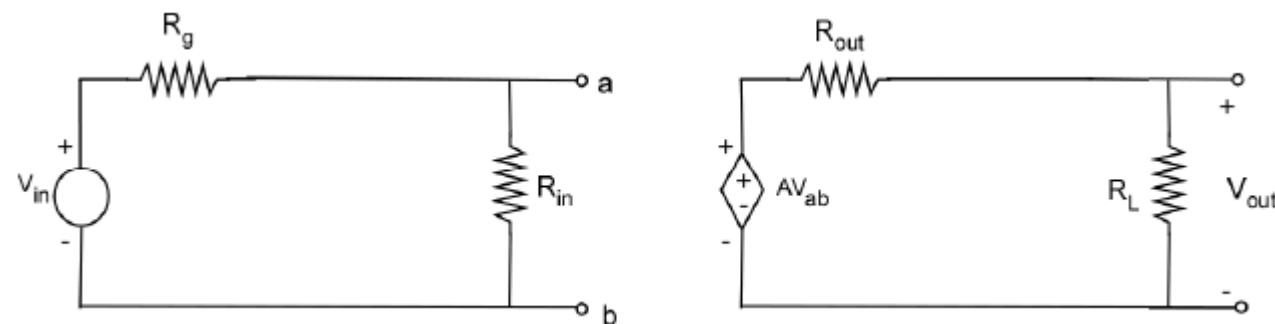**Mid-band frequency:**

- Coupling capacitors are short circuits
- Parasitic capacitors are open circuits





$$A_{MB} = \frac{v_{out}}{v_{in}}$$

$$= \frac{R_{in}}{R_{in} + R_g} A \frac{R_L}{R_L + R_{out}}$$

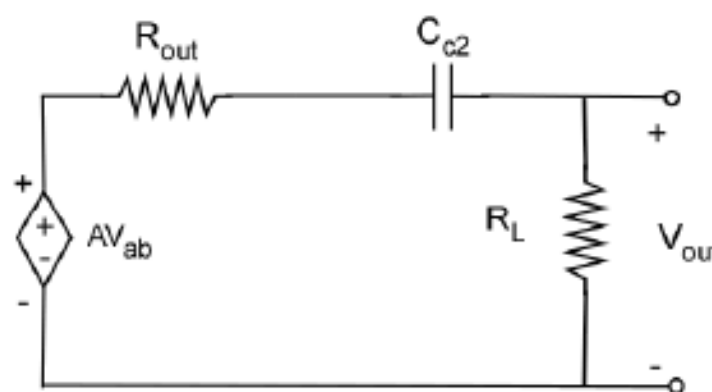
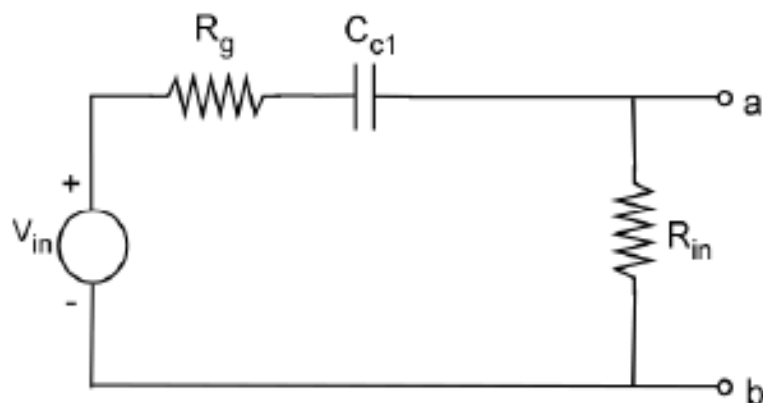
# Low frequency model

- Low frequency model:**
- Coupling capacitors are present.
  - Parasitic capacitors are open circuits.



$$\begin{aligned}
 v_{ab} &= v_{in} \frac{R_{in}}{R_{in} + R_g + \frac{1}{j\omega C_{c1}}} = v_{in} \frac{j\omega R_{in} C_{c1}}{1 + j\omega C_{c1}(R_{in} + R_g)} \\
 &= v_{in} \frac{R_{in}}{R_{in} + R_g} \frac{j\omega C_{c1}(R_{in} + R_g)}{1 + j\omega C_{c1}(R_{in} + R_g)}
 \end{aligned}$$

# Low frequency model

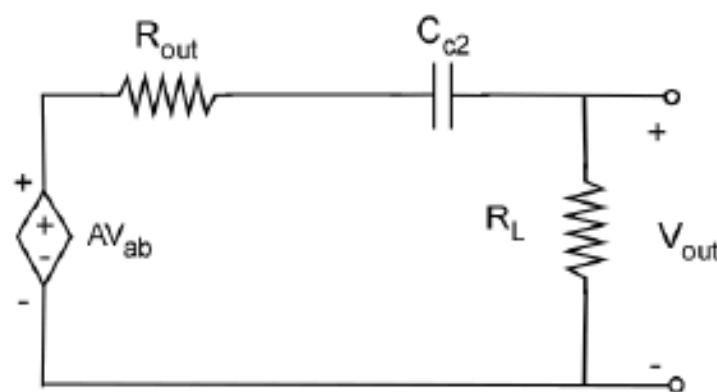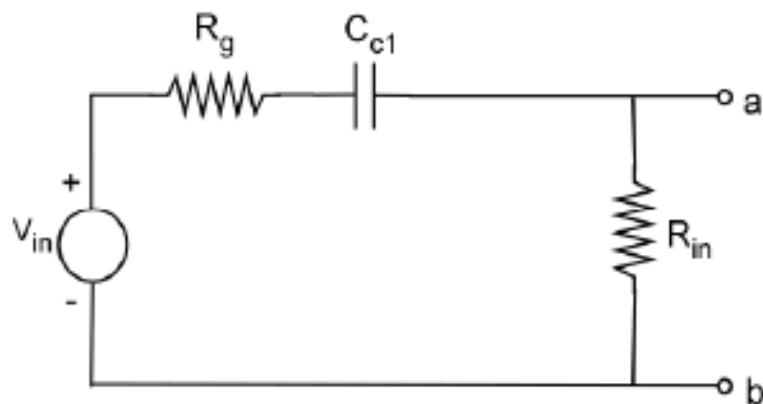


**Define:**  $f_{l1} = \frac{1}{2\pi(R_{in} + R_g)C_{c1}}$

$$f_{l2} = \frac{1}{2\pi(R_{out} + R_L)C_{c2}}$$

$$v_{ab} = v_{in} \frac{R_{in}}{R_{in} + R_g} \frac{j\omega C_{c1}(R_{in} + R_g)}{1 + j\omega C_{c1}(R_{in} + R_g)} = v_{in} \frac{R_{in}}{R_{in} + R_g} \frac{j^f / f_{l1}}{1 + j^f / f_{l1}}$$

$$v_{out} = Av_{ab} \frac{R_L}{R_L + R_{out}} \frac{j\omega C_{c2}(R_L + R_{out})}{1 + j\omega C_{c2}(R_L + R_{out})} = Av_{ab} \frac{R_L}{R_L + R_{out}} \frac{j^f / f_{l2}}{1 + j^f / f_{l2}}$$

# Low frequency model

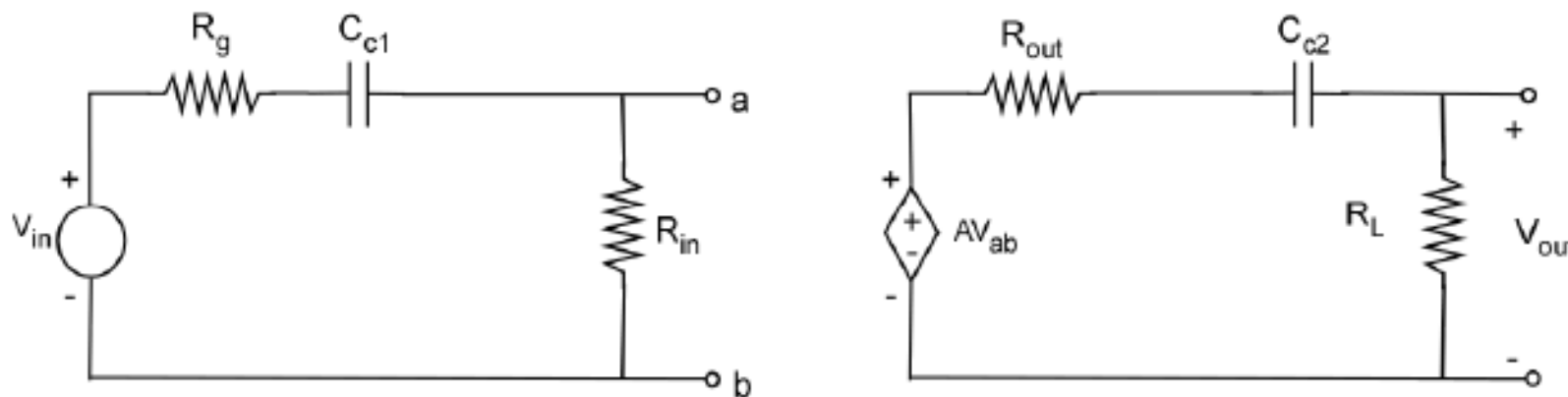



**Overall gain:** 
$$\frac{v_{out}}{v_{in}} = A \frac{R_{in}}{R_{in} + R_g} \frac{R_L}{R_L + R_{out}} \frac{j^f/f_{l1}}{1 + j^f/f_{l1}} \frac{j^f/f_{l2}}{1 + j^f/f_{l2}}$$

$$\frac{v_{out}}{v_{in}} = A_{MB} \frac{j^f/f_{l1}}{1 + j^f/f_{l1}} \frac{j^f/f_{l2}}{1 + j^f/f_{l2}}$$

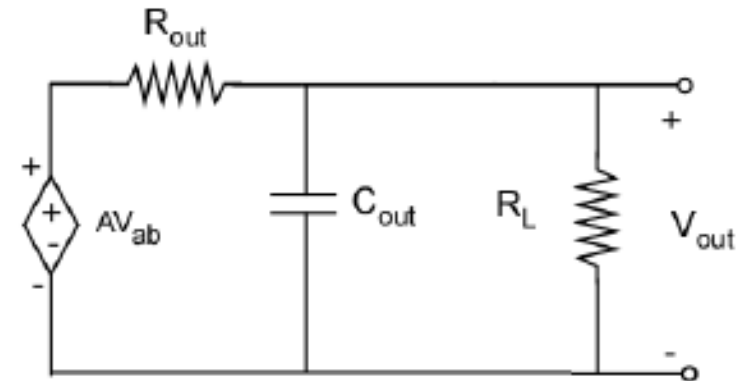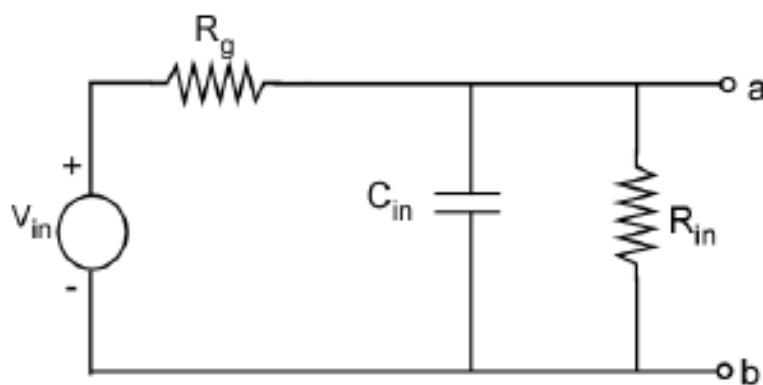
# High frequency model

*Low frequency model:*

- Coupling capacitors are short.
- Parasitic capacitors are present.




*Equivalent Thevenin Circuit*

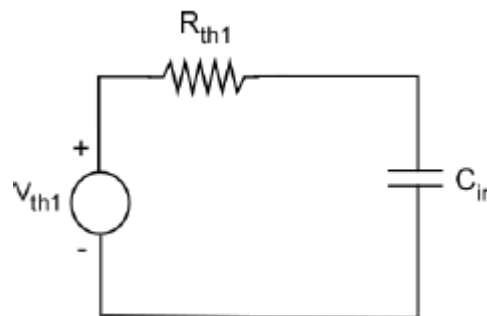

$$V_{th1} = v_{in} \frac{R_{in}}{R_{in} + R_g}$$

$$R_{th1} = R_{in} \parallel R_g$$

# High frequency model

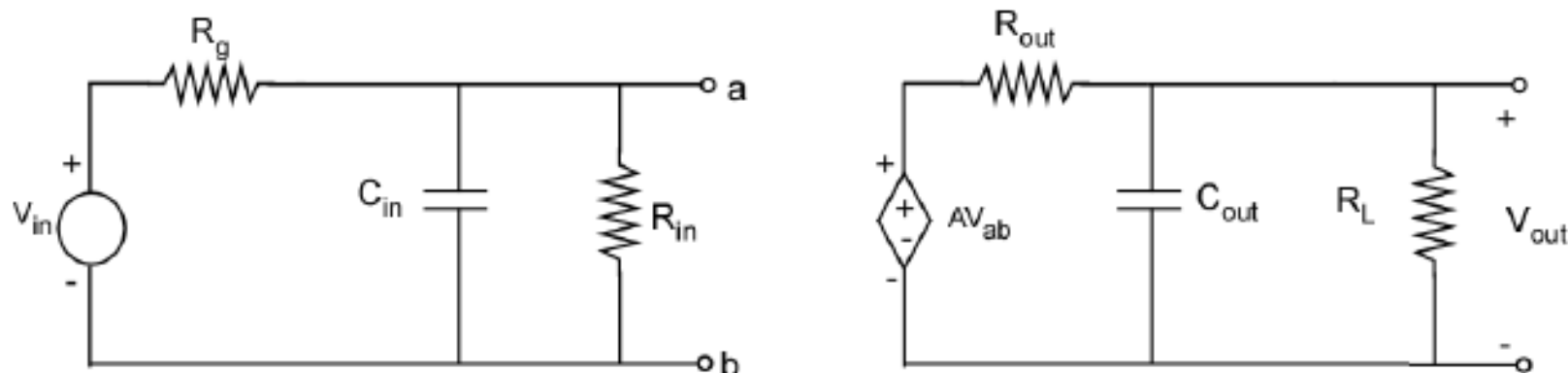



$$v_{ab} = v_{in} \frac{R_{in}}{R_{in} + R_g} \frac{1}{1 + j\omega(R_{in} \parallel R_g)C_{in}}$$

$$= v_{in} \frac{R_{in}}{R_{in} + R_g} \frac{1}{1 + jf/f_{h1}} \quad \text{where: } f_{h1} = \frac{1}{2\pi(R_{in} \parallel R_g)C_{in}}$$

$$v_{out} = Av_{ab} \frac{R_L}{R_L + R_{out}} \frac{1}{1 + j\omega C_{out}(R_L \parallel R_{out})} = Av_{ab} \frac{R_L}{R_L + R_{out}} \frac{1}{1 + jf/f_{h2}}$$

$$\text{where: } f_{h2} = \frac{1}{2\pi(R_{out} \parallel R_L)C_{out}}$$

# High frequency model

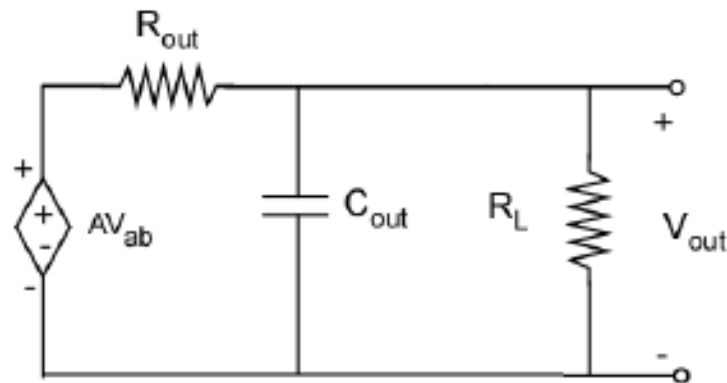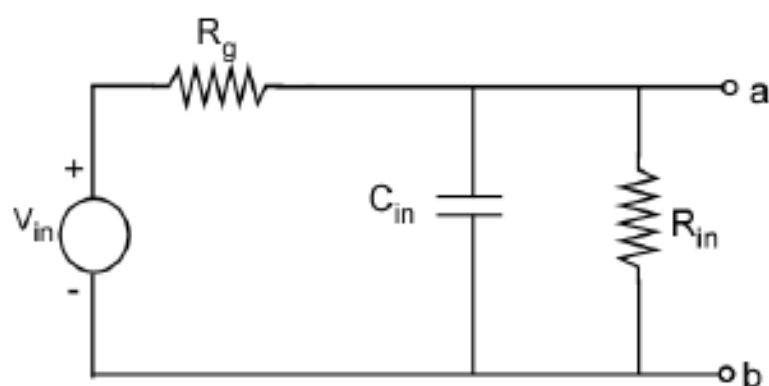

**Overall gain:** 
$$\frac{v_{out}}{v_{in}} = A v_{ab} \frac{R_{in}}{R_{in} + R_g} \frac{R_L}{R_L + R_{out}} \frac{1}{1 + jf/f_{h1}} \frac{1}{1 + jf/f_{h2}}$$

$$\frac{v_{out}}{v_{in}} = A_{MB} \frac{1}{1 + jf/f_{h1}} \frac{1}{1 + jf/f_{h2}}$$

# High frequency model

**Example 1:** Given  $R_{out} = 3k\Omega$ ,  $R_g = 200\Omega$ ,  $R_{in} = 12k\Omega$ ,  $R_L = 10k\Omega$ ,  $C_{c1} = 5\mu F$ ,  $C_{c2} = 1\mu F$ ,  $C_{in} = 200pF$ ,  $C_{out} = 40pF$ . Compute  $f_{l1}$ ,  $f_{l2}$ ,  $f_{h1}$ ,  $f_{h2}$ .

$$f_{l1} = \frac{1}{2\pi \times 12200 \times 5 \times 10^{-6}} = 2.61 \text{ Hz}$$



$$f_{l2} = \frac{1}{2\pi \times 13000 \times 1 \times 10^{-6}} = 12.2 \text{ Hz}$$

$$f_{h1} = \frac{1}{2\pi \times (12000 \parallel 200) \times 2 \times 10^{-10}} = 4.05 \text{ MHz}$$

$$f_{h2} = \frac{1}{2\pi \times (10000 \parallel 3000) \times 4 \times 10^{-11}} = 1.72 \text{ MHz}$$




# LF Response of CE Amplifier

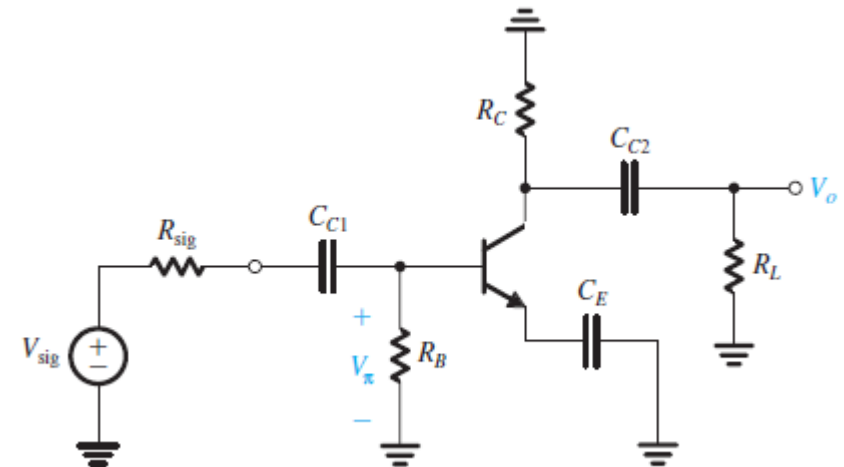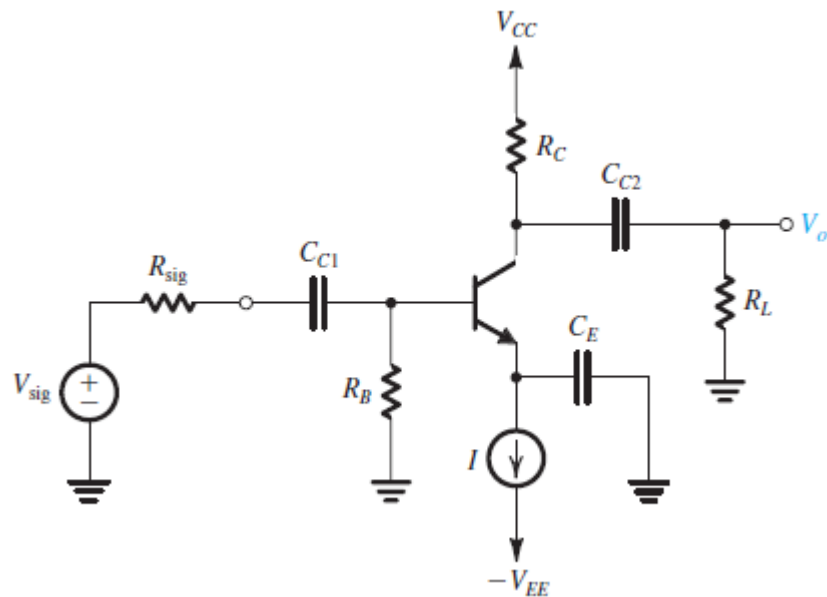
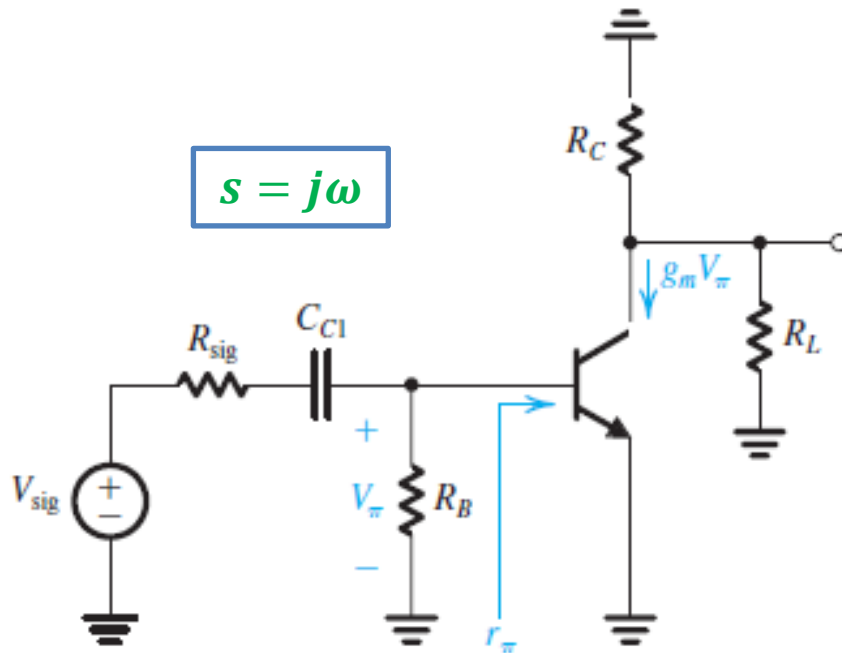
# LF Response of CE Amplifier

Considering the Effect of Each of the Three Capacitors Separately

Case 1: Consider  $C_{C1}$ , short circuit  $C_E$  and  $C_{C2}$



$$V_{\pi} = V_{sig} \frac{R_B \parallel r_{\pi}}{(R_B \parallel r_{\pi}) + R_{sig} + \frac{1}{sC_{C1}}}$$

$$V_o = -g_m V_{\pi} (R_C \parallel R_L)$$

$$\frac{V_o}{V_{sig}} = - \frac{R_B \parallel r_{\pi}}{R_B \parallel r_{\pi} + R_{sig}} g_m (R_C \parallel R_L) \times \frac{s}{s + \frac{1}{C_{C1} [R_B \parallel r_{\pi} + R_{sig}]}}$$


$$f_{P1} = \frac{1}{2\pi C_{C1} [R_B \parallel r_{\pi} + R_{sig}]}$$

$$A_{MB} = - \frac{R_B \parallel r_{\pi}}{[R_B \parallel r_{\pi} + R_{sig}]} g_m (R_C \parallel R_L)$$
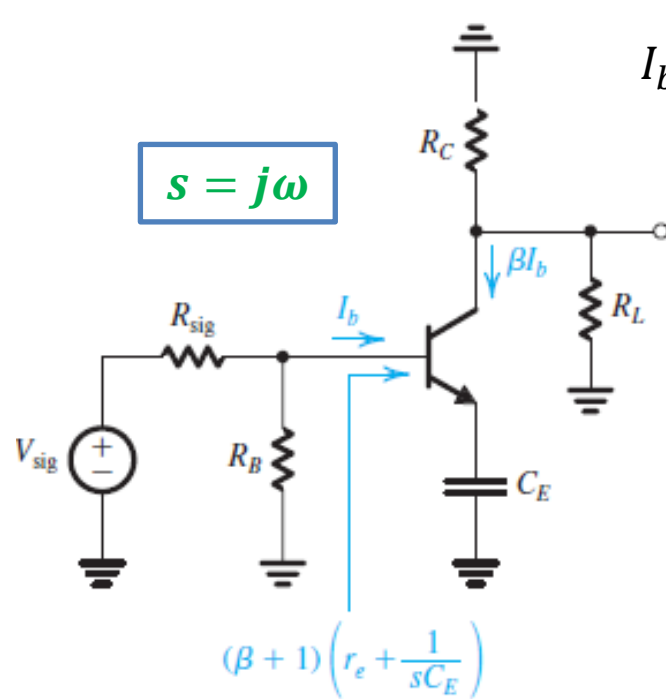
# LF Response of CE Amplifier

Considering the Effect of Each of the Three Capacitors Separately

Case 2: Consider  $C_E$ , short circuit  $C_{C1}$  and  $C_{C2}$



$$I_b = V_{sig} \frac{R_B}{R_B + R_{sig}} \frac{1}{(R_B \parallel R_{sig}) + (\beta + 1)\left(r_e + \frac{1}{sC_E}\right)}$$

$$V_o = -\beta I_b (R_C \parallel R_L)$$


$$\frac{V_o}{V_{sig}} = -\frac{R_B}{R_B + R_{sig}} \frac{\beta(R_C \parallel R_L)}{(R_B \parallel R_{sig}) + (\beta + 1)r_e} \times \frac{s}{s + \frac{1}{C_E \left[ r_e + \frac{R_B \parallel R_{sig}}{\beta + 1} \right]}}$$

$$f_{P2} = \frac{1}{2\pi C_E \left[ r_e + \frac{R_B \parallel R_{sig}}{\beta + 1} \right]}$$
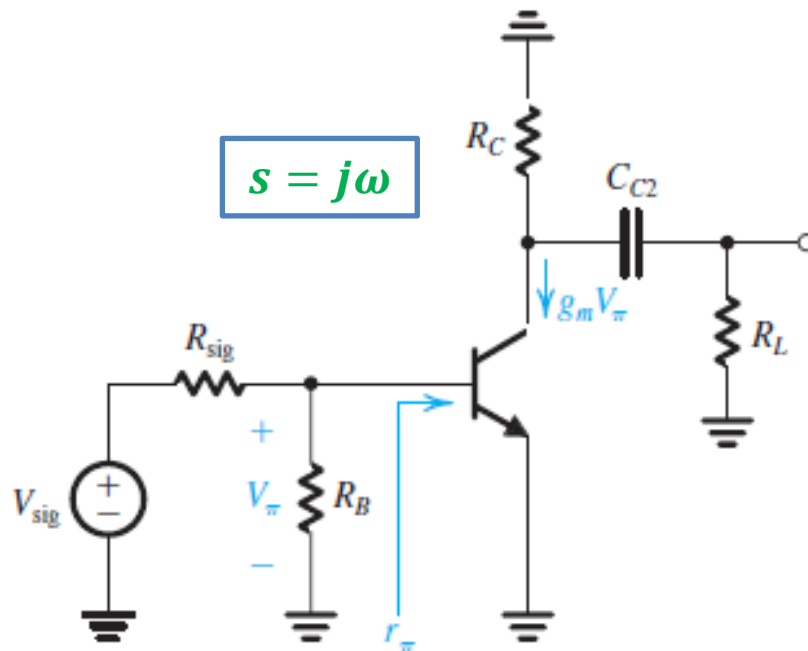
# LF Response of CE Amplifier

Considering the Effect of Each of the Three Capacitors Separately

Case 3: Consider  $C_{C2}$ , short circuit  $C_E$  and  $C_{C1}$



$$V_{\pi} = V_{sig} \frac{R_B \parallel r_{\pi}}{(R_B \parallel r_{\pi}) + R_{sig}}$$


$$V_o = -g_m V_{\pi} \frac{R_C}{R_C + \frac{1}{sC_2} + R_L} R_L$$

$$\frac{V_o}{V_{sig}} = - \frac{R_B \parallel r_{\pi}}{R_B \parallel r_{\pi} + R_{sig}} g_m (R_C \parallel R_L) \times \frac{s}{s + \frac{1}{C_{C2}(R_C + R_L)}}$$

$$f_{P3} = \frac{1}{2\pi C_{C2}(R_C + R_L)}$$


# LF Response of CE Amplifier

Case 1

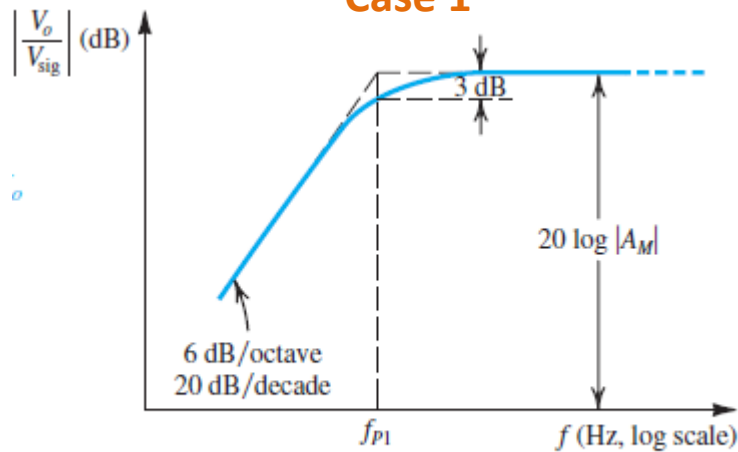


$$f_{P1} = 1/2\pi C_{C1} [(R_B \| r_\pi) + R_{sig}]$$

Case 2

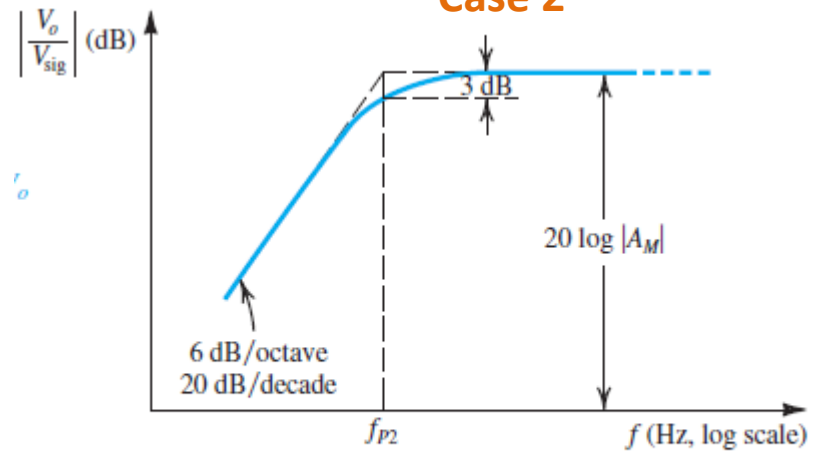


$$f_{P2} = 1/2\pi C_E \left[ r_e + \frac{R_B \| R_{sig}}{\beta + 1} \right]$$


Case 3

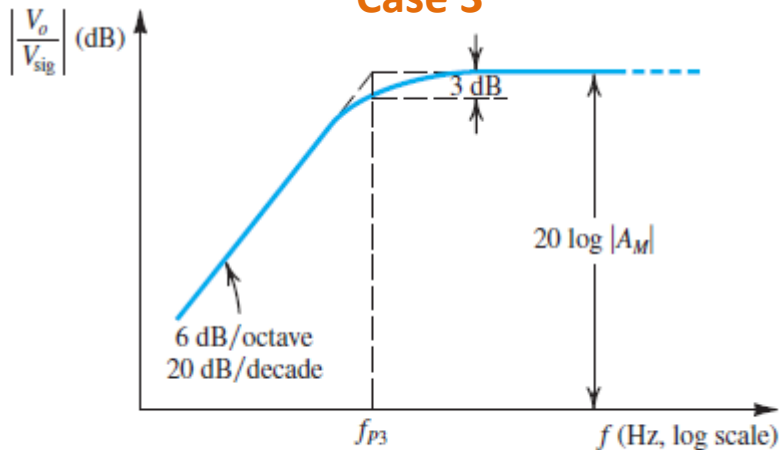

$$f_{P3} = 1/2\pi C_{C2} (R_C + R_L)$$

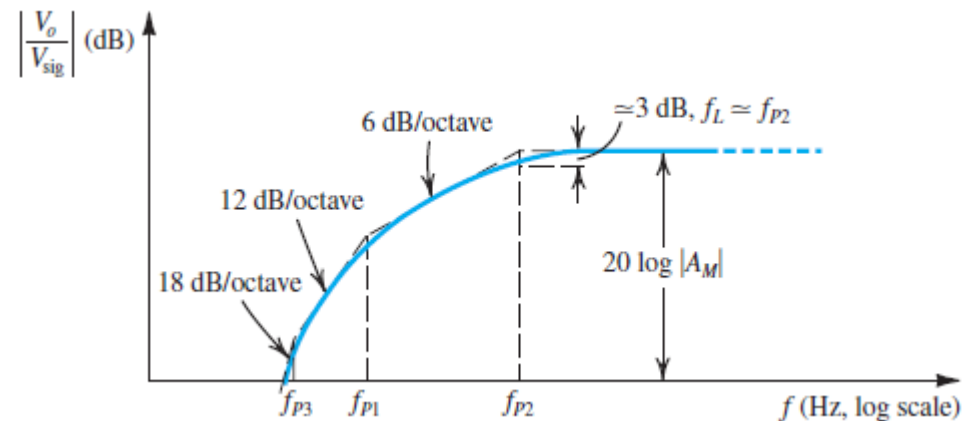

# LF Response of CE Amplifier

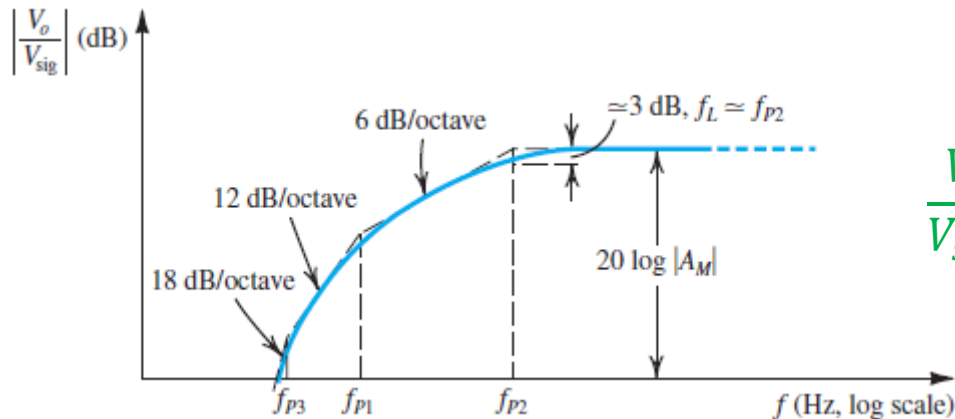



$$\frac{V_o}{V_{sig}} = -A_M \left( \frac{s}{s + \omega_{P1}} \right) \left( \frac{s}{s + \omega_{P2}} \right) \left( \frac{s}{s + \omega_{P3}} \right)$$

If  $f_{p1}$ ,  $f_{p2}$  and  $f_{p3}$  are widely separated:  $f_L = \max(f_{p1}, f_{p2}, f_{p3})$


If  $f_{p1}$ ,  $f_{p2}$  and  $f_{p3}$  are close together:  $f_L \approx \frac{1}{2\pi} \left[ \frac{1}{R_{c1}C_{c1}} + \frac{1}{R_EC_E} + \frac{1}{R_{c3}C_{c3}} \right] = f_{p1} + f_{p2} + f_{p3}$

**Example 2:** Select appropriate values for  $C_{c1}$ ,  $C_{c2}$  and  $C_E$  for the CE amplifier which has  $R_B = 100k\Omega$ ,  $R_C = 8k\Omega$ ,  $R_L = 5k\Omega$ ,  $R_{sig} = 5k\Omega$ ,  $\beta = 100$ ,  $g_m = 4mA/V$  and  $r_\pi = 2.5k\Omega$ . It is required  $f_L = 100Hz$ .

# LF Response of CS Amplifier

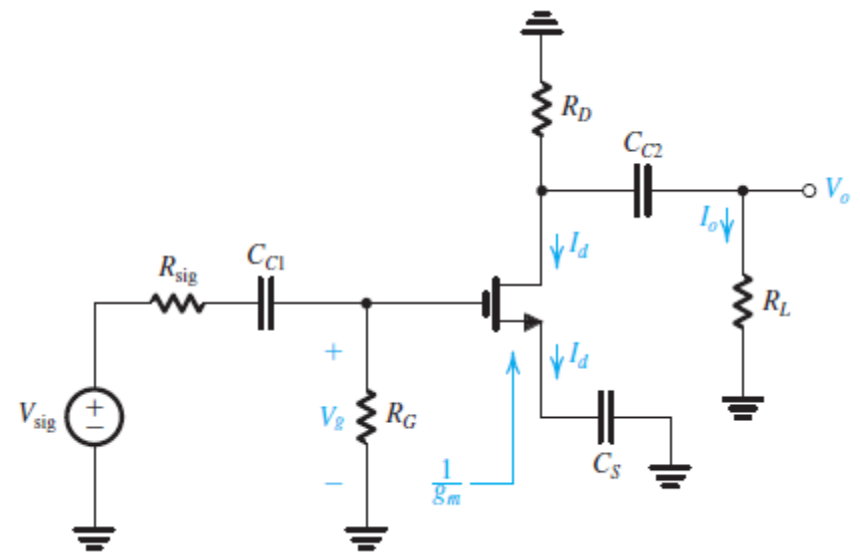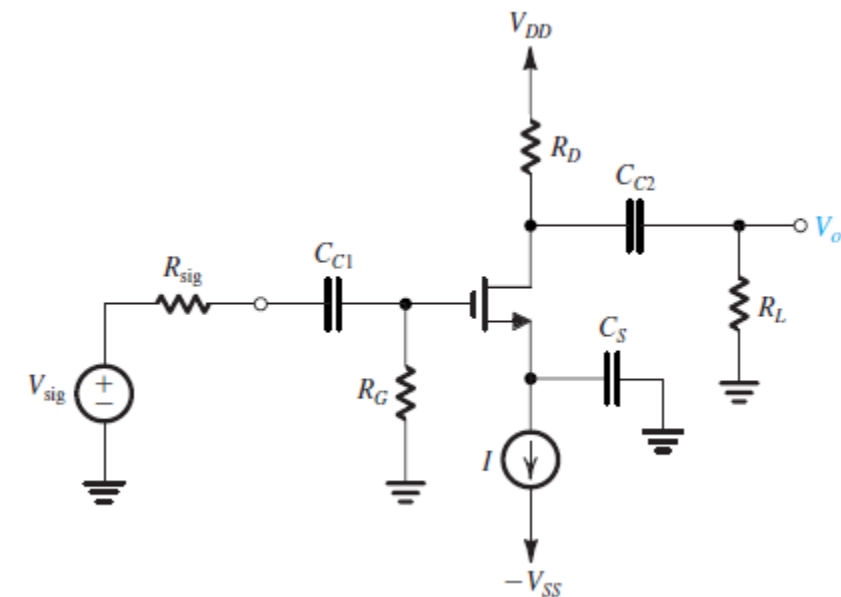

# LF Response of CS Amplifier

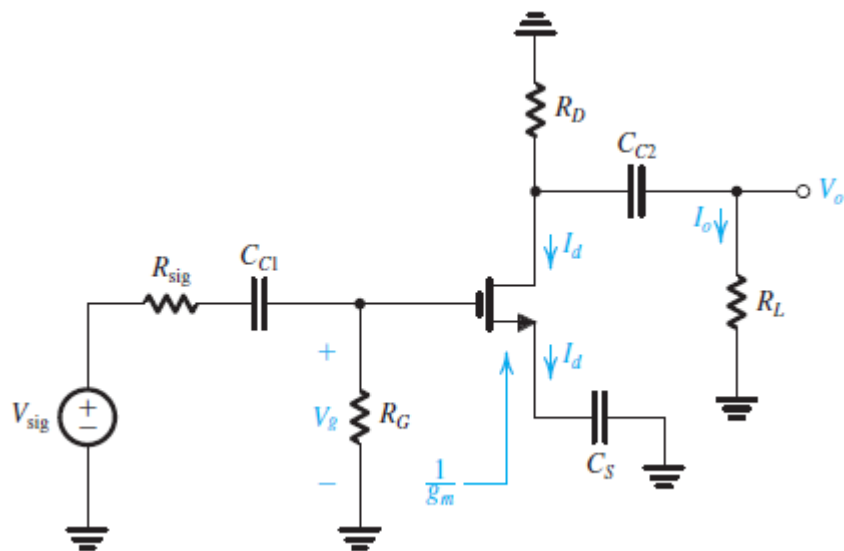

$f_{P1} = \frac{1}{2\pi C_{c1}[R_G + R_{sig}]}$
$f_{P2} = \frac{g_m}{2\pi C_S}$
$f_{P3} = \frac{1}{2\pi C_{c2}[R_D + R_L]}$

$$V_g = V_{sig} \frac{R_G}{R_G + R_{sig} + \frac{1}{sC_{c1}}}$$

$$V_g = V_{sig} \frac{R_G}{R_G + R_{sig}} \frac{s}{s + \frac{1}{C_{c1}(R_G + R_{sig})}}$$


$$I_d = \frac{V_g}{\frac{1}{g_m} + \frac{1}{sC_S}} = g_m V_g \frac{s}{s + \frac{g}{C_S}}$$

$$I_o = -I_d \frac{R_D}{R_D + R_L + \frac{1}{sC_{c2}}}$$

$$V_o = -I_d \frac{R_D R_L}{R_D + R_L} \frac{s}{s + \frac{1}{C_{c2}(R_D + R_L)}}$$



# LF Response of CS Amplifier

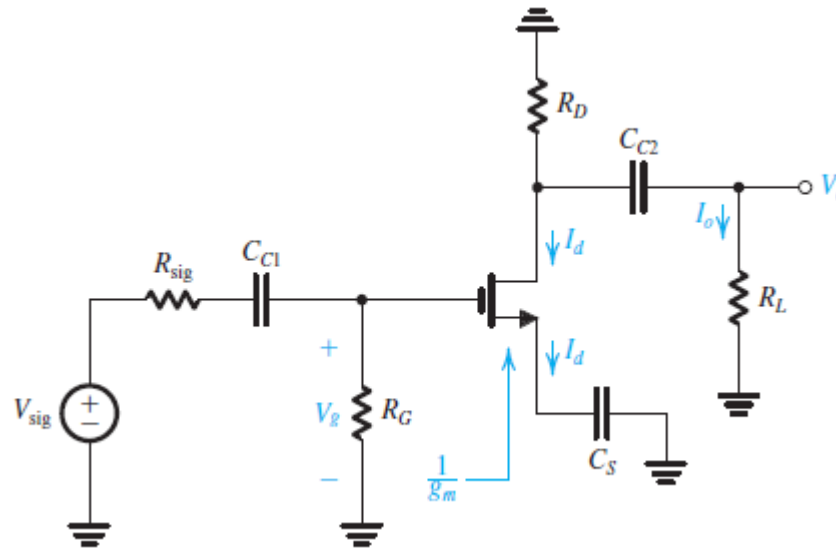

$$\frac{V_o}{V_{sig}} = -\frac{R_G}{R_G + R_{sig}} g_m (R_D \parallel R_L) \left( \frac{s}{s + \omega_{P1}} \right) \left( \frac{s}{s + \omega_{P2}} \right) \left( \frac{s}{s + \omega_{P3}} \right)$$


$$\frac{V_o}{V_{sig}} = A_{MB} \left( \frac{s}{s + \omega_{P1}} \right) \left( \frac{s}{s + \omega_{P2}} \right) \left( \frac{s}{s + \omega_{P3}} \right)$$

where:  $A_{MB} = -\frac{R_G}{R_G + R_{sig}} g_m (R_D \parallel R_L)$

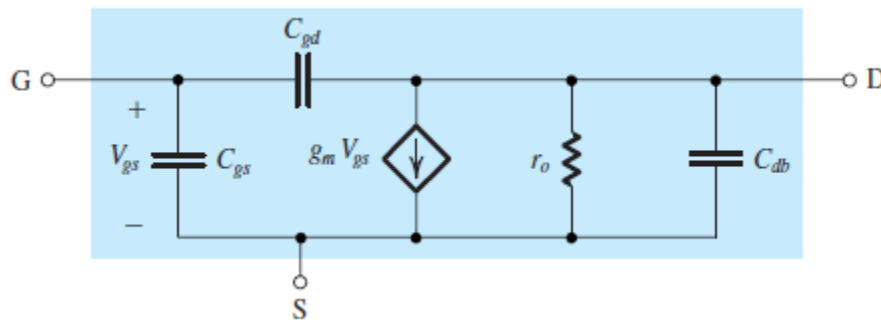
# Gate Capacitive Effect

The gate capacitive effect can be modeled by the capacitances  $C_{gs}$ ,  $C_{gd}$ .

- ❖ Triode region:  $C_{gs} = C_{gd} = \frac{1}{2}WLC_{ox}$
- ❖ Saturation region:  $C_{gs} = \frac{2}{3}WLC_{ox}$   $C_{gd} = 0$
- ❖ Cutoff region:  $C_{gs} = 0$   $C_{gd} = 0$




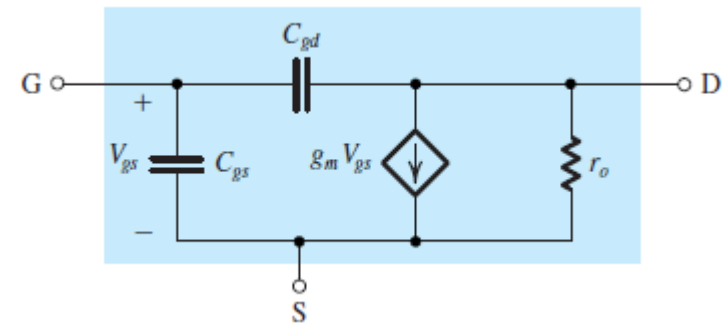*Equivalent circuit for the case in which the source is connected to the substrate*




*Equivalent circuit with  $C_{db}$  neglected (to simplify analysis)*


# HF Response of CS Amplifier

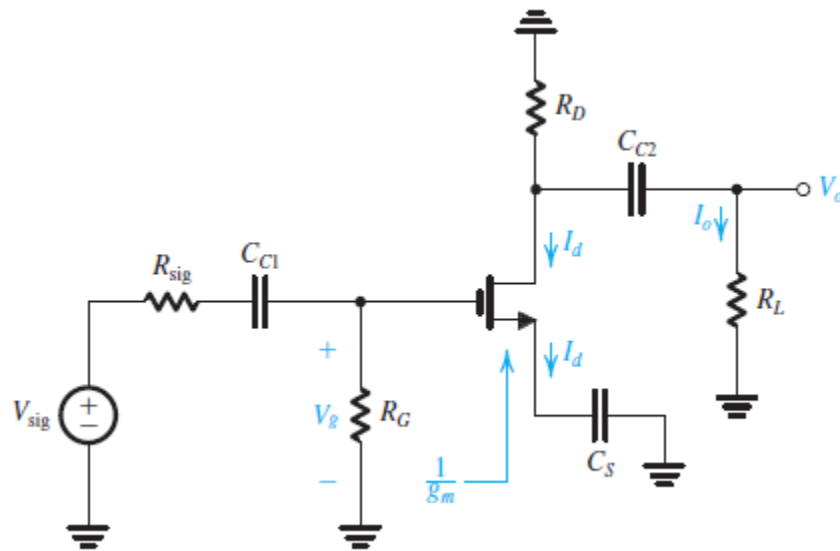

CS Amplifier

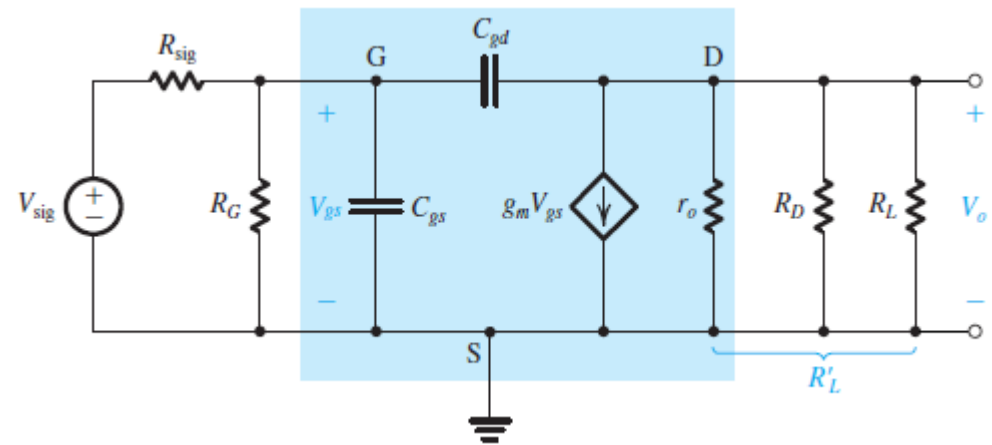


HF Equivalent circuit

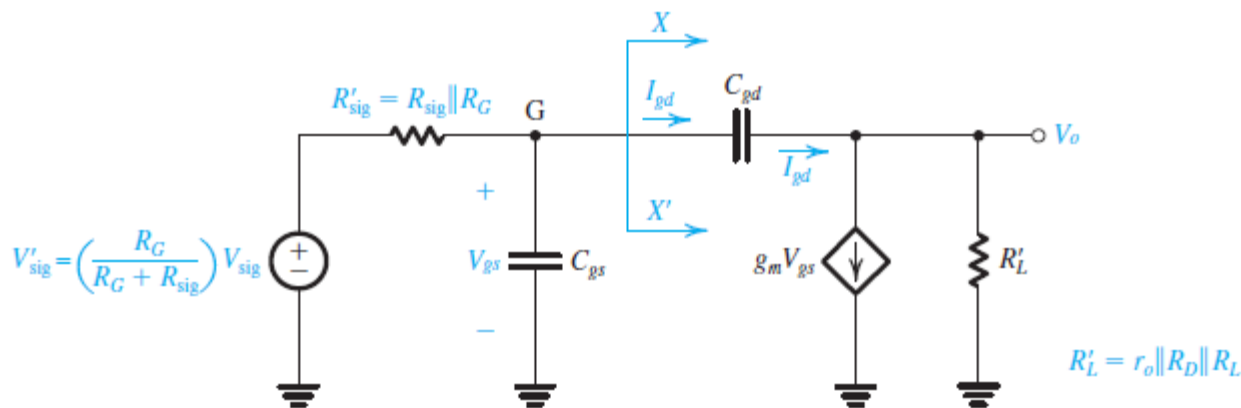

Simplified HF Equivalent circuit

# HF Response of CS Amplifier

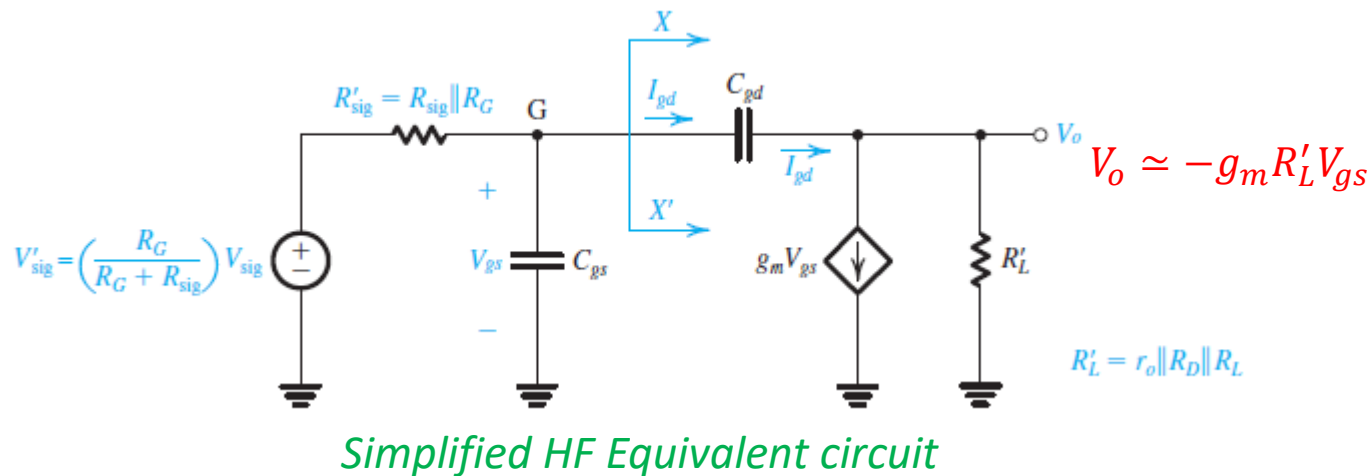

Midband gain: 
$$A_{MB} = \frac{V_o}{V_{sig}} = -\frac{R_G}{R_G + R_{sig}} (g_m R'_L)$$

Load current: 
$$I'_L = g_m V_{gs} - I_{gd}$$

At frequencies in the vicinity of  $f_H$ :  $I'_L \approx g_m V_{gs} \rightarrow V_o \approx -g_m R'_L V_{gs}$


The current  $I_{gd}$  can now be found as: 
$$I_{gd} = sC_{gd}(V_{gs} - V_o) = sC_{gd}(V_{gs} + g_m R'_L V_{gs})$$
  

$$= sC_{gd}(1 + g_m R'_L)V_{gs}$$
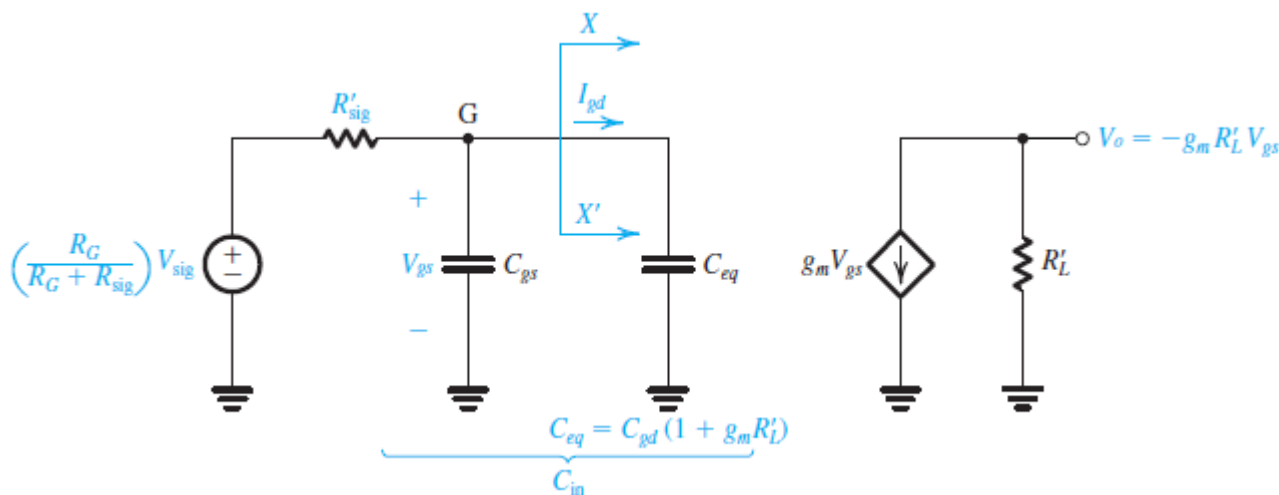
# HF Response of CS Amplifier

❖ Therefore, the left hand side of  $XX'$  could be replaced by  $C_{eq}$ , where

$$sC_{eq}V_{gs} = sC_{gd}(1 + g_m R'_L)V_{gs} \quad \text{or} \quad \mathbf{C_{eq} = C_{gd}(1 + g_m R'_L)}$$



**Miller effect**

$$C_{in} = C_{gs} + C_{eq} = C_{gs} + C_{gd}(1 + g_m R'_L)$$

$$R'_{sig} = R_{sig} \parallel R_G$$

# HF Response of CS Amplifier


$V_{gs}$  can be written as:

$$V_{gs} = \left( \frac{R_G}{R_G + R_{sig}} V_{sig} \right) \frac{1}{1 + \frac{jf}{f_0}} = \left( \frac{R_G}{R_G + R_{sig}} V_{sig} \right) \frac{1}{1 + \frac{s}{\omega_0}}$$

where  $f_0$  is the 3dB frequency:  $f_0 = \frac{1}{2\pi C_{in} R'_{sig}}$


$$C_{in} = C_{gs} + C_{eq} = C_{gs} + C_{gd}(1 + g_m R'_L)$$

$$R'_{sig} = R_{sig} \parallel R_G$$

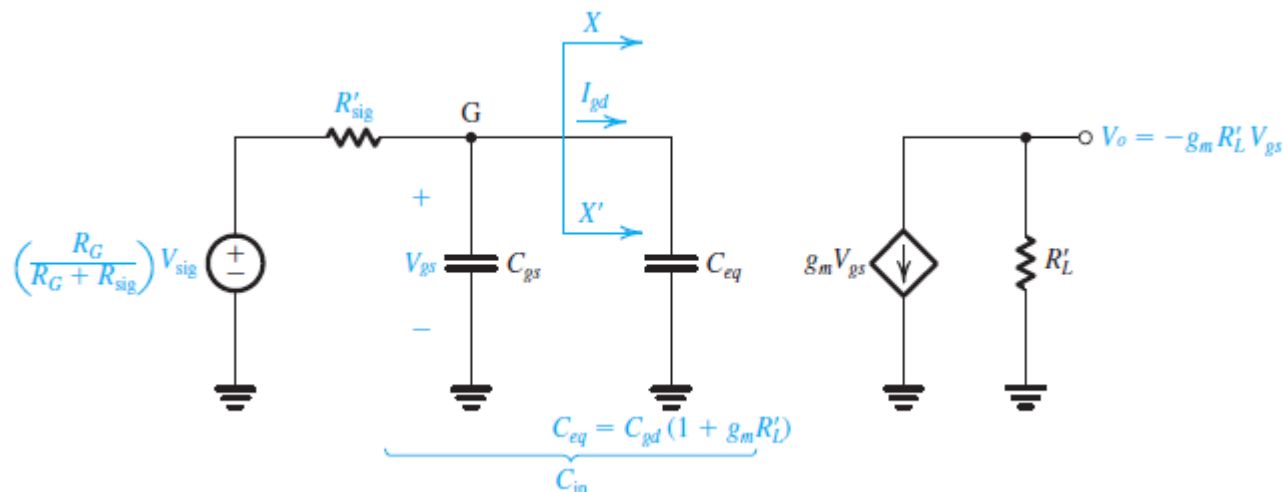


# HF Response of CS Amplifier

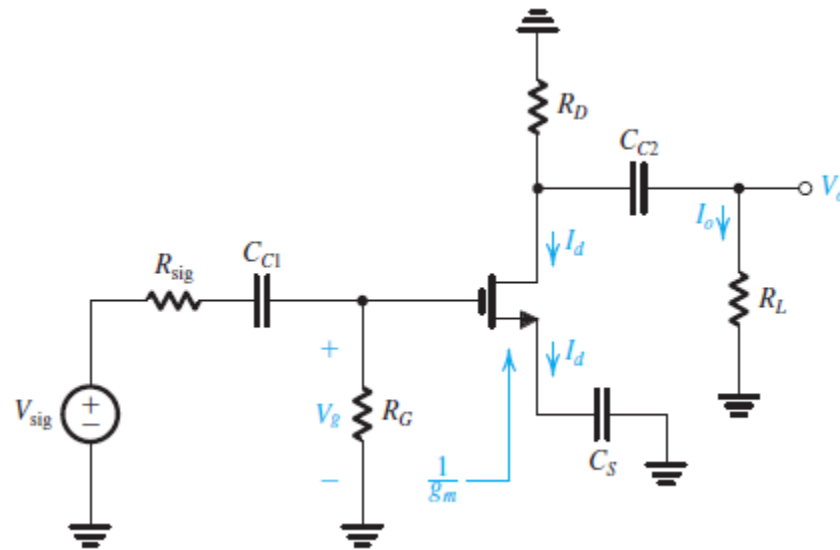**Example 3:** Find the mid-band gain  $A_{MB}$  and the upper 3-dB frequency  $f_H$  of a CS amplifier fed with a signal source having an internal resistance  $R_{sig} = 100k\Omega$ . The amplifier has  $R_G = 4.7M\Omega$ ,  $R_D = R_L = 15k\Omega$ ,  $g_m = 1mA/V$ ,  $r_o = 150k\Omega$ ,  $C_{gs} = 1pF$ ,  $C_{gd} = 0.4pF$ .




# BJT High Frequency model

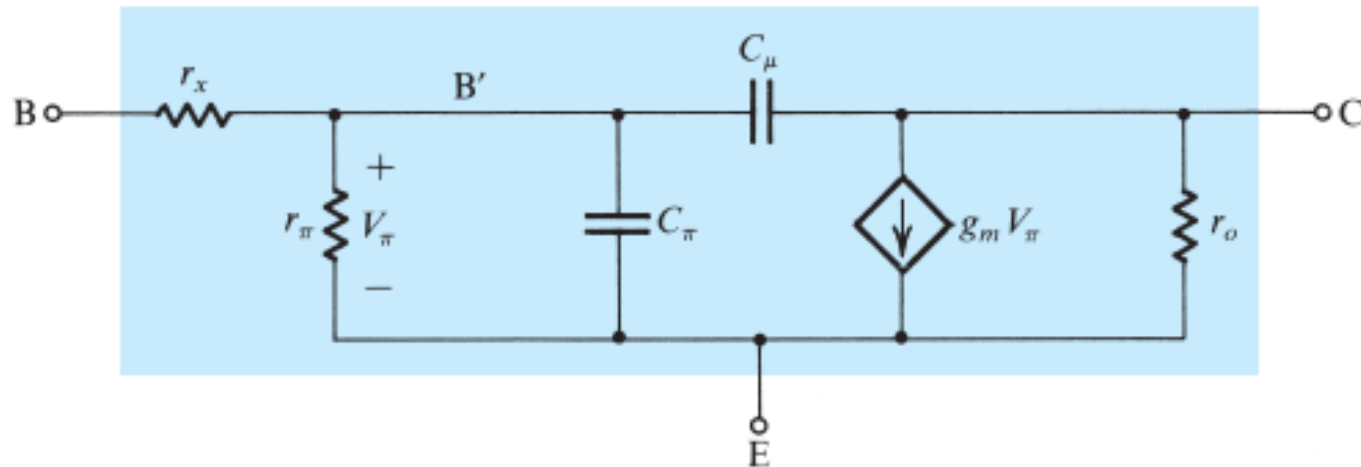

*Emitter-base capacitance  $C_{\pi}$  is in the range of a few picofarads.*



*Collector-base capacitance  $C_{\mu}$  is in the range of a fraction of pF to a few pF.*

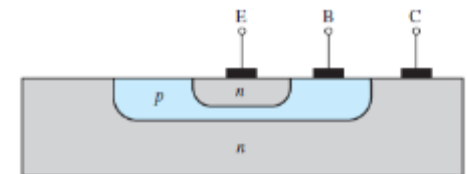$r_x$  is added to model the resistance of the silicon material of the base region between the base terminal B and a fictitious internal, or intrinsic, base terminal that is right under the emitter region.





# HF Response of CE Amplifier

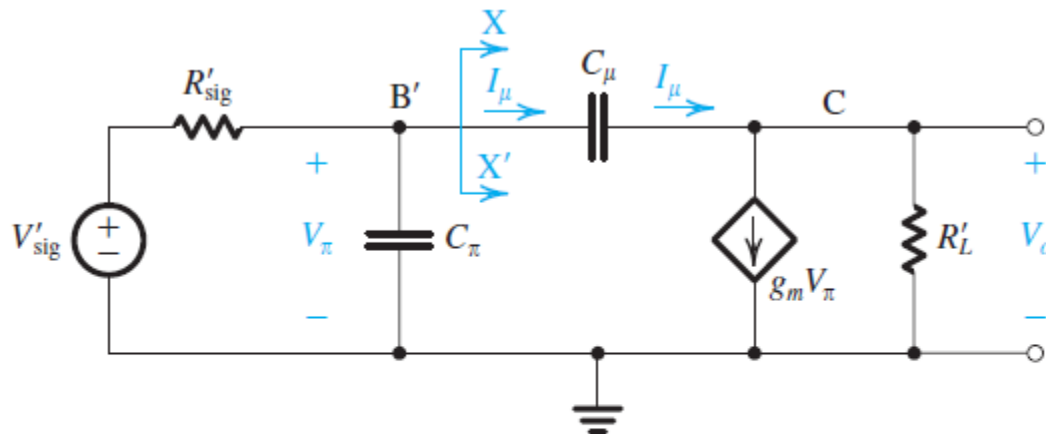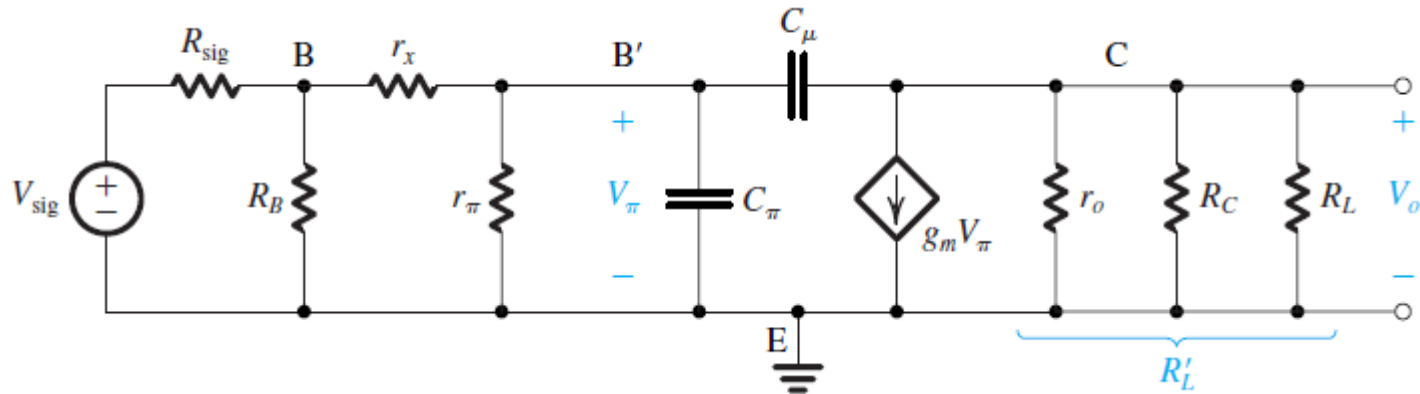


$$V'_{\text{sig}} = V_{\text{sig}} \frac{R_B}{R_B + R_{\text{sig}}} \frac{r_{\pi}}{r_{\pi} + r_x + (R_{\text{sig}} \parallel R_B)}$$

$$R'_L = r_o \parallel R_C \parallel R_L$$

$$R'_{\text{sig}} = r_{\pi} \parallel [r_x + (R_B \parallel R_{\text{sig}})]$$

# HF Response of CE Amplifier

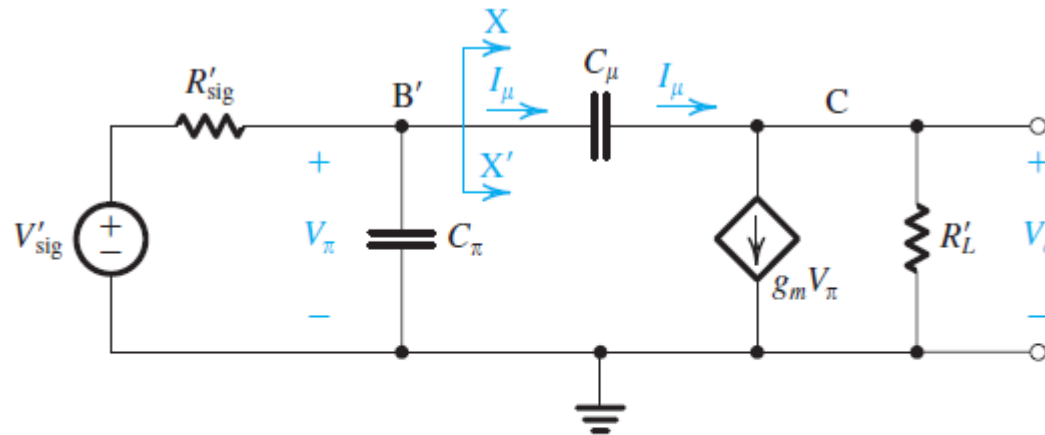

$$V'_{sig} = V_{sig} \frac{R_B}{R_B + R_{sig}} \frac{r_\pi}{r_\pi + r_x + (R_{sig} \parallel R_B)}$$

$$R'_L = r_o \parallel R_C \parallel R_L$$

$$R'_{sig} = r_\pi \parallel [r_x + (R_B \parallel R_{sig})]$$


Midband gain:

$$A_{MB} = \frac{V_o}{V_{sig}} = - \frac{R_B}{R_B + R_{sig}} \frac{r_\pi}{r_\pi + r_x + R_B \parallel R_{sig}} (g_m R'_L)$$

And:

$$\frac{V_o}{V_{sig}} = A_{MB} \frac{1}{1 + \frac{jf}{f_0}}$$

# HF Response of CE Amplifier

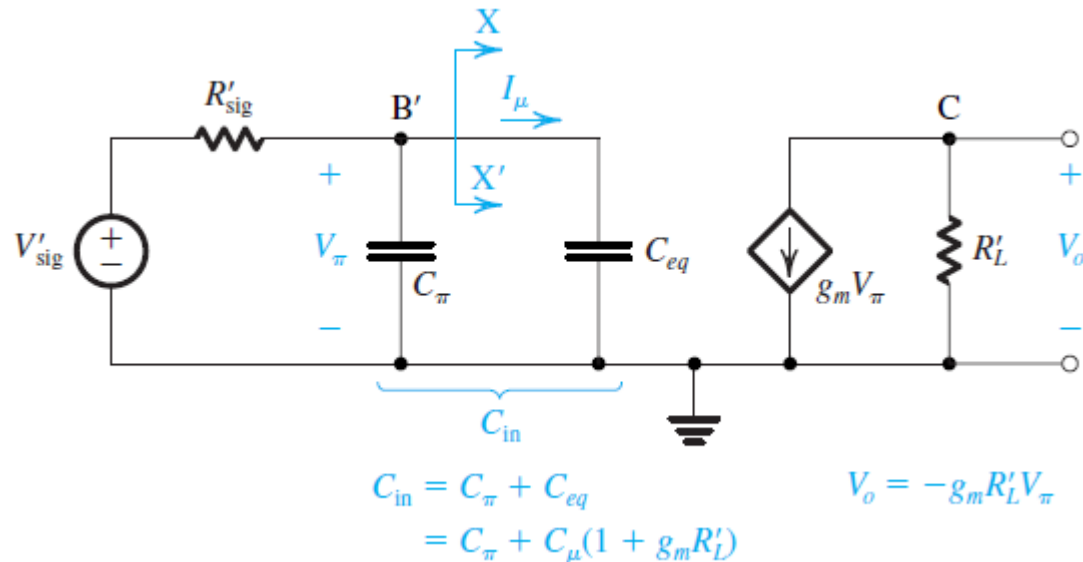

the 3dB frequency:  $f_0 = \frac{1}{2\pi C_{in} R'_{sig}}$


Miller effect

$$C_{in} = C_{\pi} + C_{eq} = C_{\pi} + C_{\mu}(1 + g_m R'_L)$$

$$R'_{sig} = R_{sig} \parallel R_G$$

# HF Response of CE Amplifier

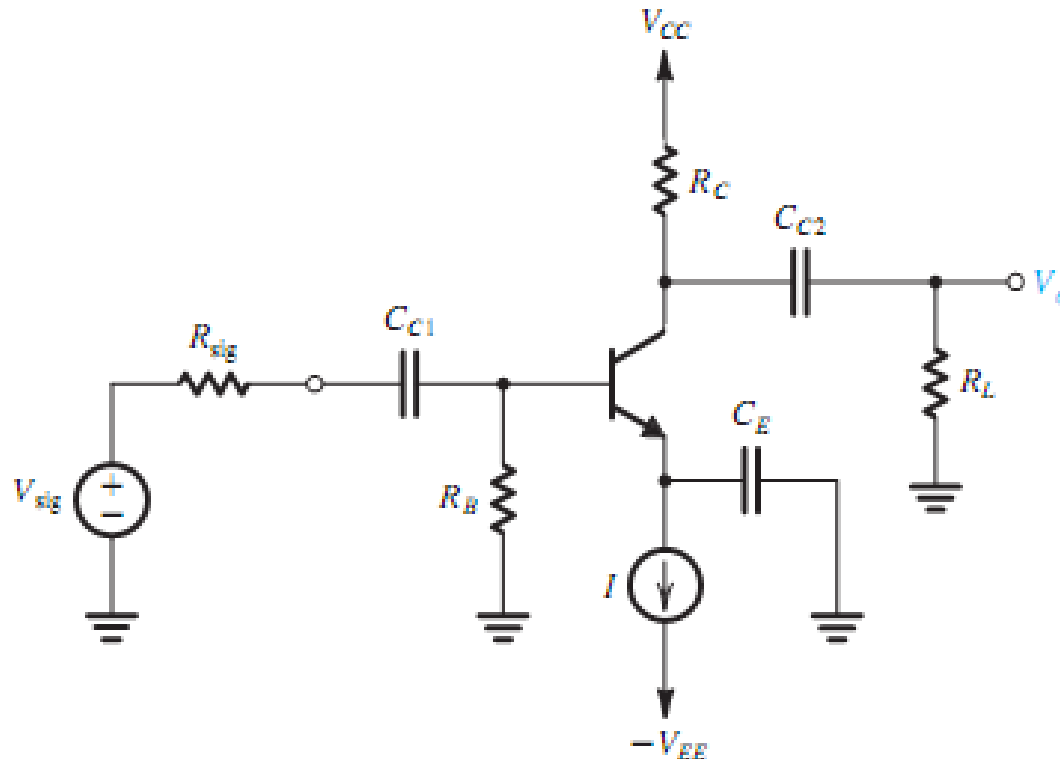**Example 4:** It is required to find the mid-band gain and the upper 3-dB frequency of the common-emitter amplifier. Given:  $V_{CC} = V_{EE} = 10V$ ,  $I = 1mA$ ,  $R_B = 100k\Omega$ ,  $R_{sig} = 5k\Omega$ ,  $R_L = 5k\Omega$ ,  $\beta_0 = 100$ ,  $V_A = 100V$ ,  $C_\mu = 1pF$ ,  $C_\pi = 7pF$  and  $r_x = 50\Omega$ .




# Miller's Theorem

In the analysis of HF response of CE and CS amplifiers, a technique for replacing the bridging capacitance by an equivalent input capacitance.

This technique is based on a general theorem known as **Miller's theorem**.

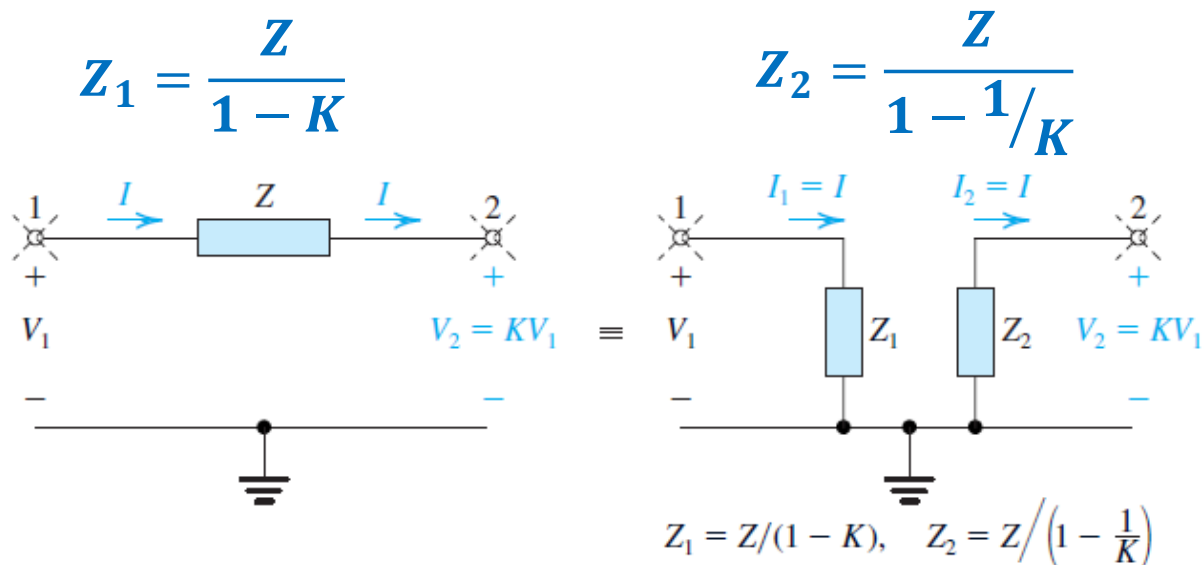
Assume that  $V_2 = KV_1$ . Miller's theorem states that impedance  $Z$  can be replaced by two impedances:



# Miller's Theorem

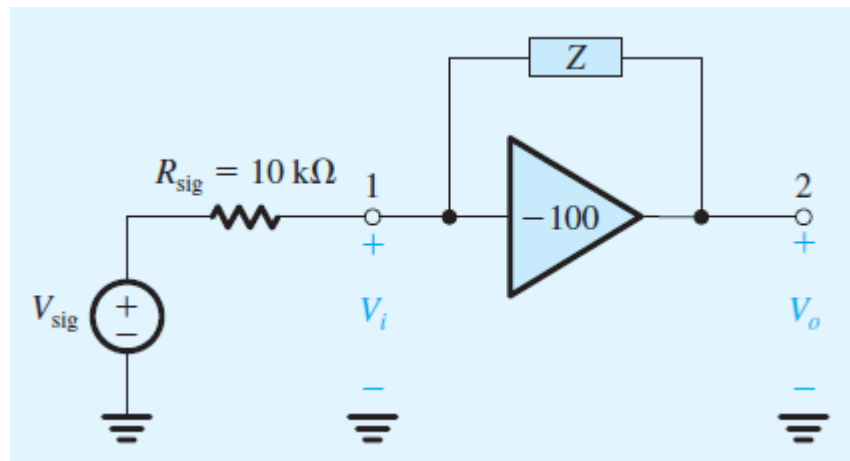**Example 5:** An ideal voltage amplifier having a gain of  $-100V/V$  with an impedance  $Z$  connected between its output and input terminals. Find the Miller equivalent circuit when  $Z$  is

- A  $1M\Omega$  resistance.
- a  $1pF$  capacitance. In each case, use the equivalent circuit to determine  $V_o/V_{sig}$ .




# Analyzing using Miller's theorem

The value of and can be determined using Miller's theorem:


$$C_1 = C_{gd}(1 - K)$$

$$C_2 = C_{gd} \left(1 - 1/K\right)$$

where:  $K = V_o / V_{gs} = -g_m R'_L$

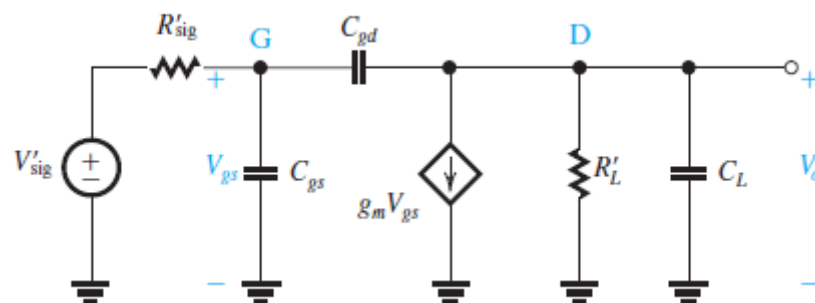

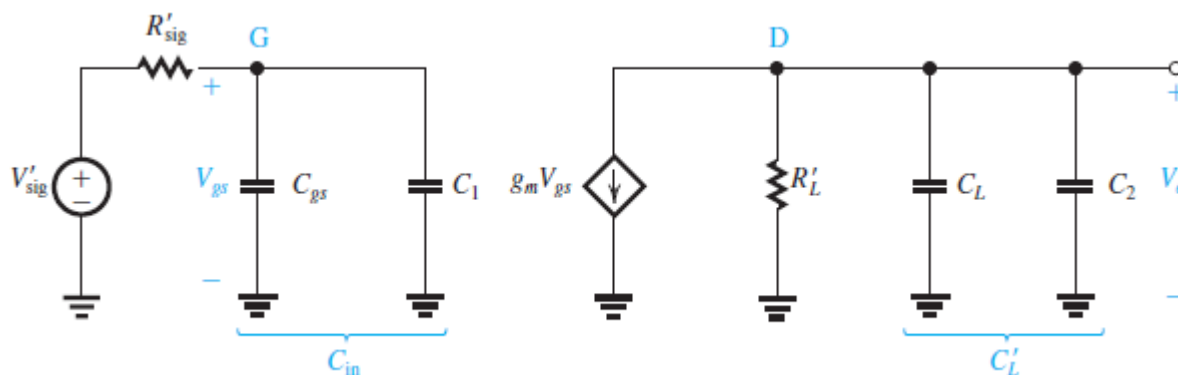Generalized HF equivalent circuit for the CS amplifier



HF equivalent circuit model of the CS amplifier  
after the application of Miller's theorem

# Analyzing using Miller's theorem

$C_1$  and  $C_2$  will be used to determine the overall transfer function.

$$C_1 = C_{gd}(1 - K) = C_{gd}(1 + g_m R'_L) \quad C_2 = C_{gd} \left(1 - 1/K\right) = C_{gd} \left(1 + 1/g_m R'_L\right)$$

At the input side:


$$f_{hi} = \frac{1}{2\pi(C_{gs} + C_1)R'_{sig}}$$

At the output side:

$$f_{ho} = \frac{1}{2\pi(C_{gs} + C_2)R'_L}$$

The approximated transfer function:
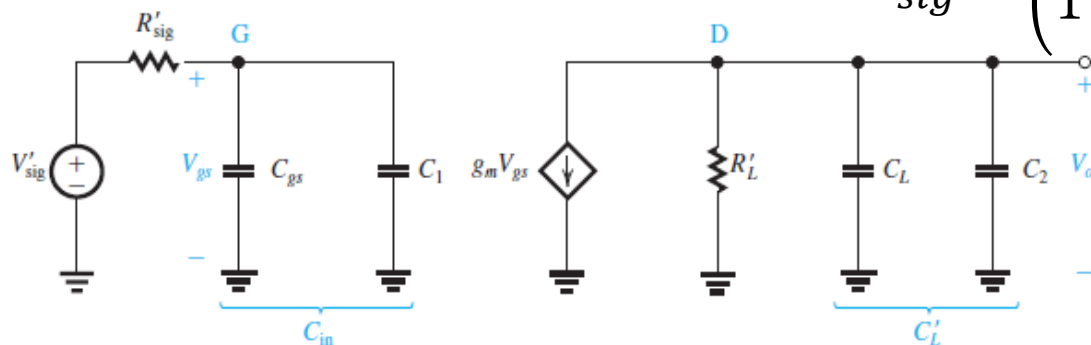
$$\frac{V_o}{V'_{sig}} = \frac{-g_m R'_L}{\left(1 + \frac{s}{\omega_{hi}}\right)\left(1 + \frac{s}{\omega_{ho}}\right)}$$



HF equivalent circuit model of the CS amplifier  
after the application of Miller's theorem

$$f_H = \frac{1}{\sqrt{\frac{1}{f_{hi}^2} + \frac{1}{f_{ho}^2}}}$$



# The HF Gain Function

The amplifier gain can be expressed in the general form:  $A(s) = A_M F_H(s)$

where: 
$$F_H(s) = \frac{(1 + s/\omega_{z1})(1 + s/\omega_{z2}) \dots (1 + s/\omega_{zn})}{(1 + s/\omega_{p1})(1 + s/\omega_{p2}) \dots (1 + s/\omega_{pn})}$$

The designer needs to estimate the value of the upper 3-dB frequency  $f_H$   
→ particularly interested in the part of the HF band close to the midband.

*If the dominant pole exists:* 
$$F_H(s) \approx \frac{1}{(1 + s/\omega_{p1})}$$

*If the dominant pole does not exist:* For simplicity, consider the following case:

$$F_H(s) = \frac{(1 + s/\omega_{z1})(1 + s/\omega_{z2})}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$

# The HF Gain Function

The magnitude of  $f_H$  can be written as:

$$|F_H(j\omega)|^2 = \frac{(1 + \omega^2/\omega_{z1}^2)(1 + \omega^2/\omega_{z2}^2)}{(1 + \omega^2/\omega_{p1}^2)(1 + \omega^2/\omega_{p2}^2)}$$

By definition  $\omega = \omega_H$ .  $|F_H|^2 = \frac{1}{2}$ , thus:

$$\frac{1}{2} = \frac{(1 + \omega^2/\omega_{z1}^2)(1 + \omega^2/\omega_{z2}^2)}{(1 + \omega^2/\omega_{p1}^2)(1 + \omega^2/\omega_{p2}^2)}$$

Since  $\omega_H < \omega_P, \omega_Z$ , we can neglect  $\omega_H^4$ :  $\omega_H \approx 1 / \sqrt{\frac{1}{\omega_{p1}^2} + \frac{1}{\omega_{p2}^2} - \frac{2}{\omega_{z1}^2} - \frac{2}{\omega_{z2}^2}}$

This relationship can be extended to any number of poles and zeros:


$$\omega_H \approx 1 / \sqrt{\left( \frac{1}{\omega_{p1}^2} + \frac{1}{\omega_{p2}^2} + \dots \right) - \left( \frac{2}{\omega_{z1}^2} + \frac{2}{\omega_{z2}^2} + \dots \right)}$$

# The HF Gain Function

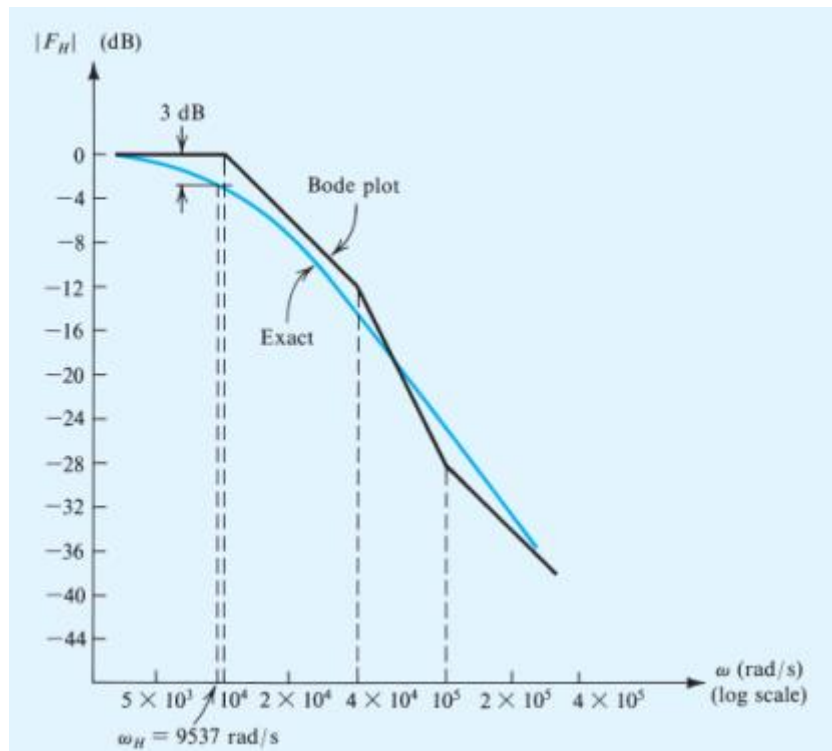**Example 6:** The high-frequency response of an amplifier is characterized by the transfer function:

$$F_H(s) = \frac{1 - s/10^5}{(1 + s/10^4)(1 + s/4 \times 10^5)}$$

Determine the 3-dB frequency approximately and exactly.




# Analyzing using Exact Method

Node equation at the drain provides:

$$sC_{gd}(V_{gs} - V_o) = g_m V_{gs} + \frac{V_o}{R'_L} + sC_L V_o$$
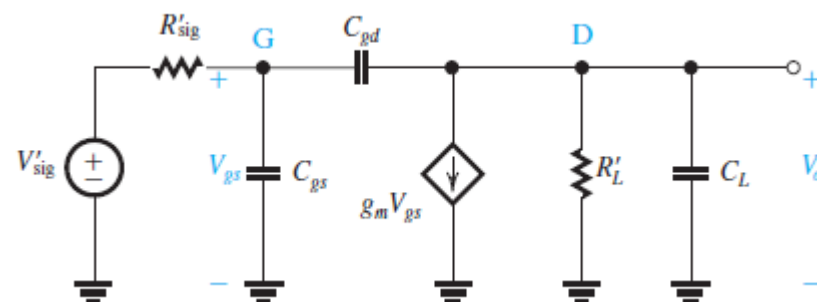
$$\rightarrow V_{gs} = \frac{-V_o}{g_m R'_L} \frac{1 + s(C_L + C_{gd})R'_L}{1 - sC_{gd}/g_m}$$




Generalized HF equivalent circuit for the CS amplifier

Node equation at G provides:

$$I_i = sC_{gs}V_{gs} + sC_{gd}(V_{gs} - V_o)$$

Then:
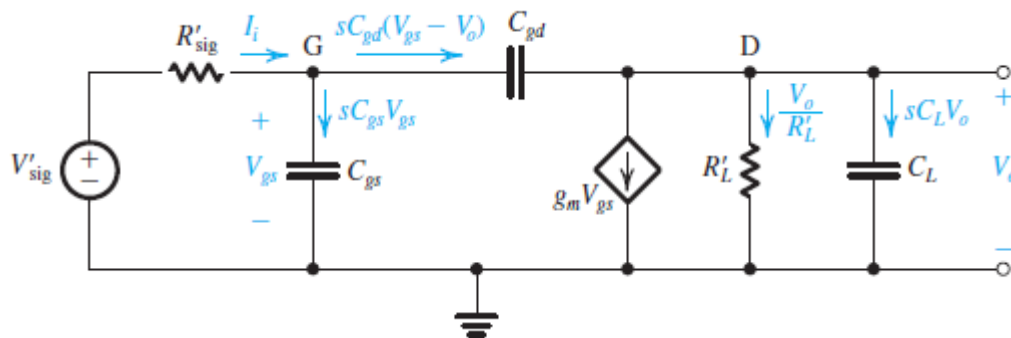
$$V'_{sig} = V_{gs} \left[ 1 + s(C_{gs} + C_{gd})R'_{sig} \right] - sC_{gs}R'_{sig}V_o$$




# Analyzing using Exact Method

The amplifier gain is: 
$$\frac{V_o}{V'_{sig}} = \frac{-g_m R'_L [1 - s C_{gd} / g_m]}{1 + s \mathbf{A} + s^2 \mathbf{B}}$$

where: 
$$\mathbf{A} = [C_{gs} + C_{gd}(1 + g_m R'_L)] R'_{sig} + (C_L + C_{gd}) R'_L$$

$$\mathbf{B} = [(C_L + C_{gd}) C_{gs} + C_L C_{gd}] R'_{sig} R'_L$$

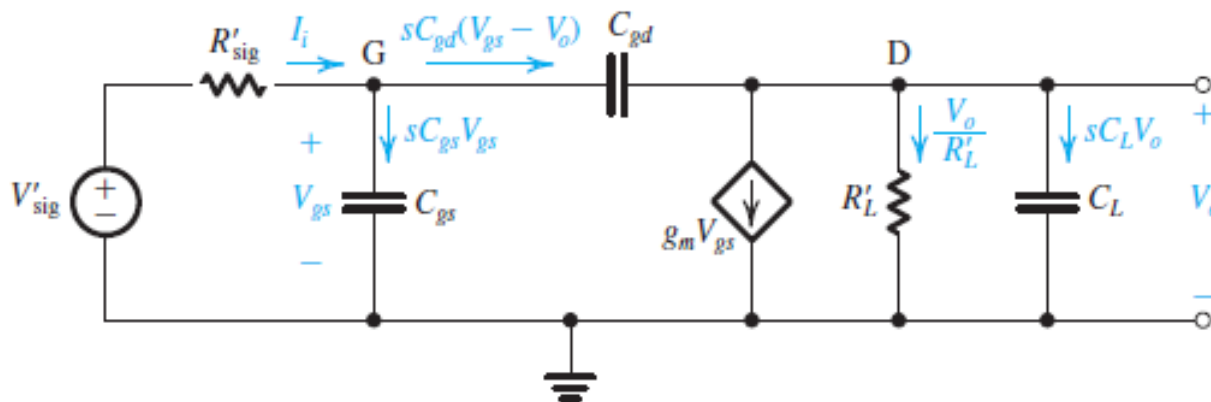The transfer function has a **second-order denominator**, and thus the amplifier has two poles. Also the **numerator is of the first order**.



# Analyzing using Exact Method

The amplifier gain is: 
$$\frac{V_o}{V'_{sig}} = \frac{-g_m R'_L [1 - s C_{gd} / g_m]}{1 + sA + s^2 B}$$

Zeros:  $\omega_{P1} = \infty$        $\omega_{P2} = g_m / C_{gd}$

Poles: the denominator polynomial  $D(s)$  can be expressed as:

$$D(s) = \left(1 + \frac{s}{\omega_{P1}}\right) \left(1 + \frac{s}{\omega_{P2}}\right) = 1 + s \left(\frac{1}{\omega_{P1}} + \frac{1}{\omega_{P2}}\right) + \frac{s^2}{\omega_{P1} \omega_{P2}}$$

$$\approx 1 + s \frac{1}{\omega_{P1}} + s^2 \frac{1}{\omega_{P1} \omega_{P2}}$$

This gives:  $\omega_{P1} \approx \frac{1}{A} = \frac{1}{[C_{gs} + C_{gd}(1 + g_m R'_L)] R'_{sig} + (C_L + C_{gd}) R'_L}$

$$\omega_{P2} = \frac{1}{B} = \frac{[C_{gs} + C_{gd}(1 + g_m R'_L)] R'_{sig} + (C_L + C_{gd}) R'_L}{[(C_L + C_{gd}) C_{gs} + C_L C_{gd}] R'_{sig} R'_L}$$

# Analyzing using Exact Method

**Example 7:** Consider an IC CS amplifier for which  $g_m = 1.25\text{mA/V}^2$ ,  $C_{gs} = 20\text{fF}$ ,  $C_{gd} = 5\text{fF}$ ,  $C_L = 25\text{fF}$ ,  $R'_{sig} = 10\text{k}\Omega$ ,  $R'_L = 10\text{k}\Omega$ .

Determine  $f_H$  using


- the Miller approximation.
- Miller's theorem.
- Determine the frequencies of the two poles and the zero and hence the 3-dB frequency.

# HF Response of the CG Amplifiers
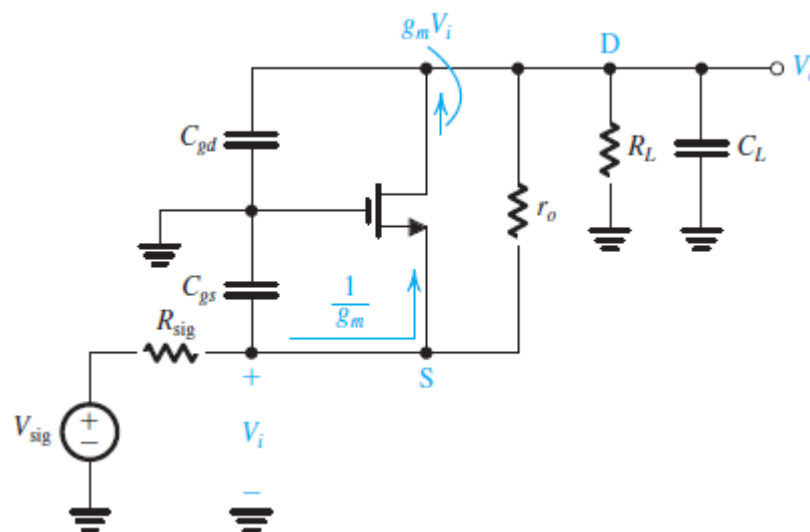
## ❖ CS and CE amplifier:

- Substantial gain at mid-band frequencies.
- Low  $f_H$  due to the large input capacitance  $C_{in}$  (Miller effect).

→ In order to obtain wide bandwidth: need circuit configurations that do not suffer from the Miller effect: Common Gate (CG) circuit.





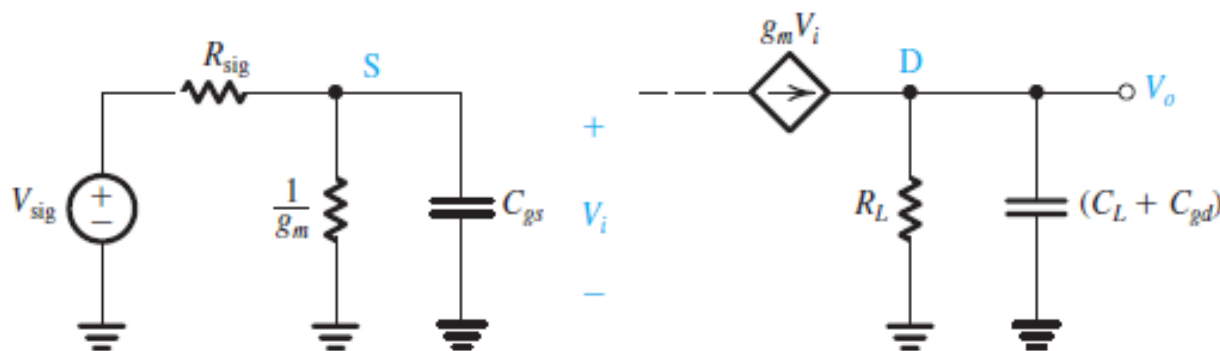
# HF Response of the CG Amplifiers

*If  $r_o$  is neglected: the circuit is greatly simplified.*

Two poles:  $f_{P1} = \frac{1}{2\pi C_{gs} \left( R_{sig} \parallel \frac{1}{g_m} \right)}$   $f_{P2} = \frac{1}{2\pi R_L (C_{gs} + C_L)}$




*If  $r_o$  is not neglected: reading Ref. page 746-750.*

# HF Response of the Source and Emitter Amplifiers


**Major advantage of the source follower:** its excellent high-frequency response.

**Midband gain:** 
$$A_M = \frac{(R_L \parallel r_o)}{(R_L \parallel r_o) + \frac{1}{g_m}}$$

$$R_o = \frac{1}{g_m} \parallel r_o$$

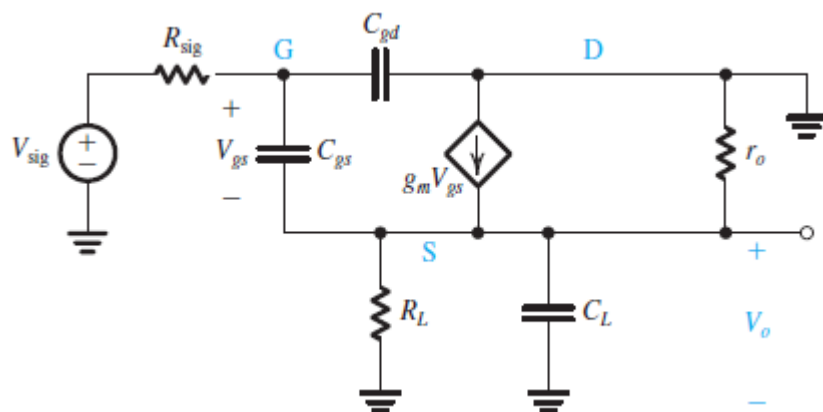

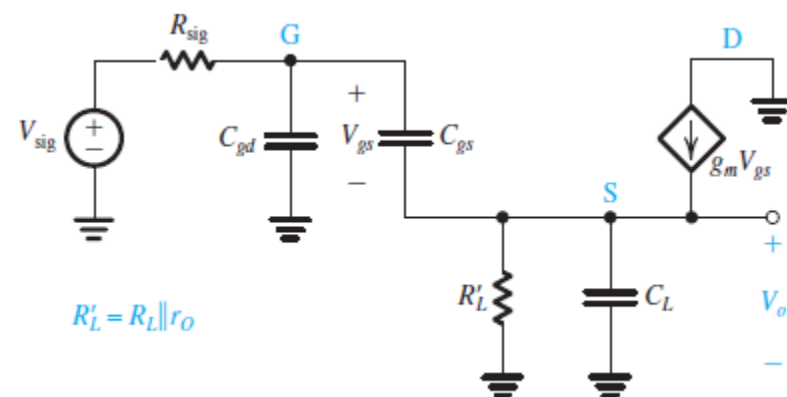*Equivalent circuit of Source Follower Amplifier*



*Simplified equivalent circuit of Source Follower Amplifier*


# Exercises

**Exercise 4:** The following figure shows the high-frequency equivalent circuit of a CS amplifier with a resistance  $R_s$  connected in the source lead. The purpose of this problem is to show that the value of  $R_s$  can be used to control the gain and bandwidth of the amplifier, specifically to allow the designer to trade gain for increased bandwidth.

a. Derive an expression for the low-frequency voltage gain.

b. Derive  $R_{gs}$  and  $R_{gd}$ .

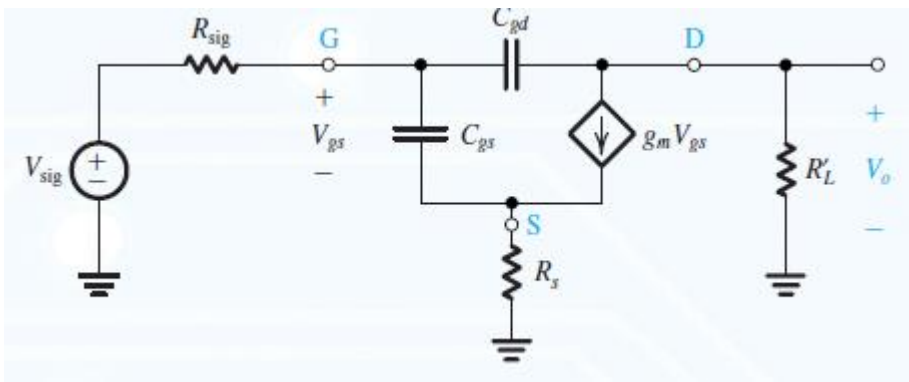c. Let  $R_{sig} = 100k\Omega$ ,  $g_m = 4mA/V$ ,  $R'_L = 5k\Omega$ ,  $C_{gs} = C_{gd} = 1pF$ . Determine the low frequency gain and 3dB frequency  $f_H$  for 3 cases:  $R_s = 0$ ,  $R_s = 100\Omega$  and,  $R_s = 250\Omega$ . Comment.




$$R_s = 0: A_v = -20, f_H = 72kHz$$

$$R_s = 100: A_v = -14.3, f_H = 99kHz$$


$$R_s = 250: A_v = -10, f_H = 137kHz$$

# A1 - BJT High Frequency model

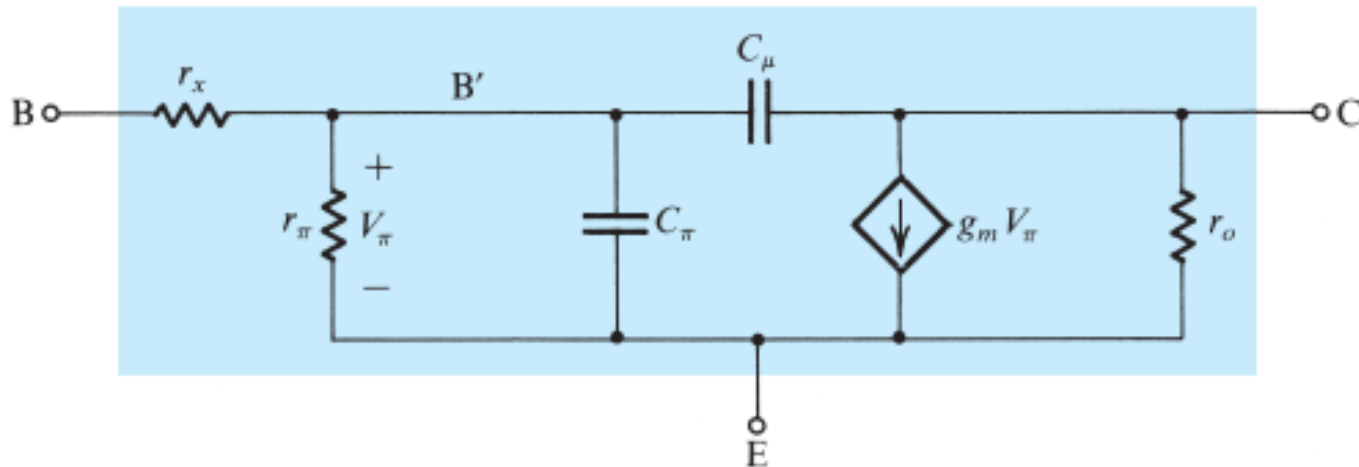

- ❖ The transistor data sheets **do not usually specify** the value of  $C_\pi$ .
- ❖ Rather, the behavior of  $\beta$  (or  $h_{fe}$ ) **versus frequency** is normally **given**.
- ❖ **Need** to derive an expression for  $h_{fe}$  to determine  $C_\pi$  and  $C_\mu$

# A1 - BJT High Frequency model

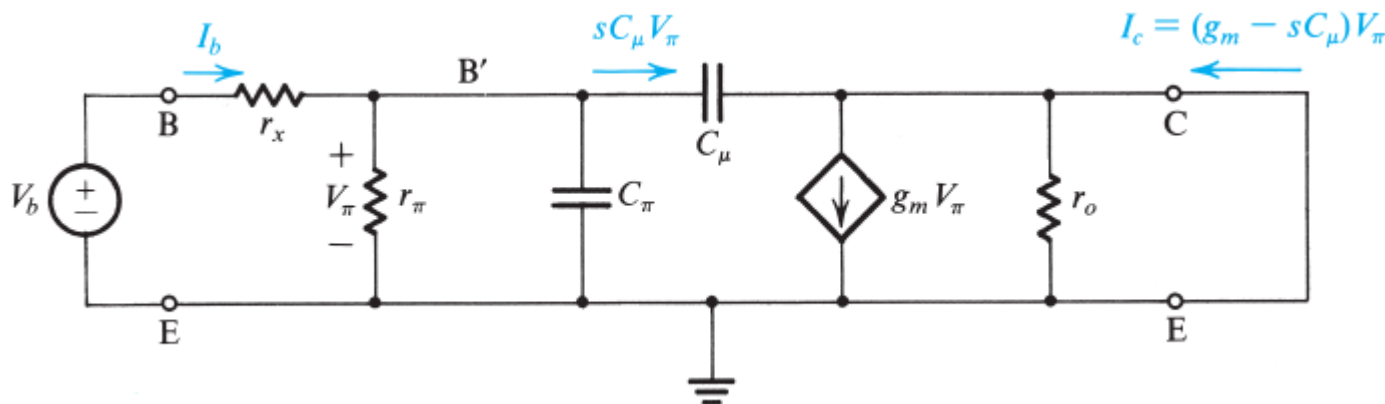

The short-circuit collector current  $I_c$  can be written as:  $I_c = (g_m - sC_\mu)V_\pi$

And 
$$V_\pi = I_b(r_\pi \parallel C_\pi \parallel C_\mu) = \frac{I_b}{1/r_\pi + sC_\pi + sC_\mu}$$

Then 
$$h_{fe} \equiv \frac{I_c}{I_b} = \frac{(g_m - sC_\mu)}{1/r_\pi + sC_\pi + sC_\mu} \approx \frac{g_m r_\pi}{1 + s(C_\pi + C_\mu)r_\pi}$$

Q&A