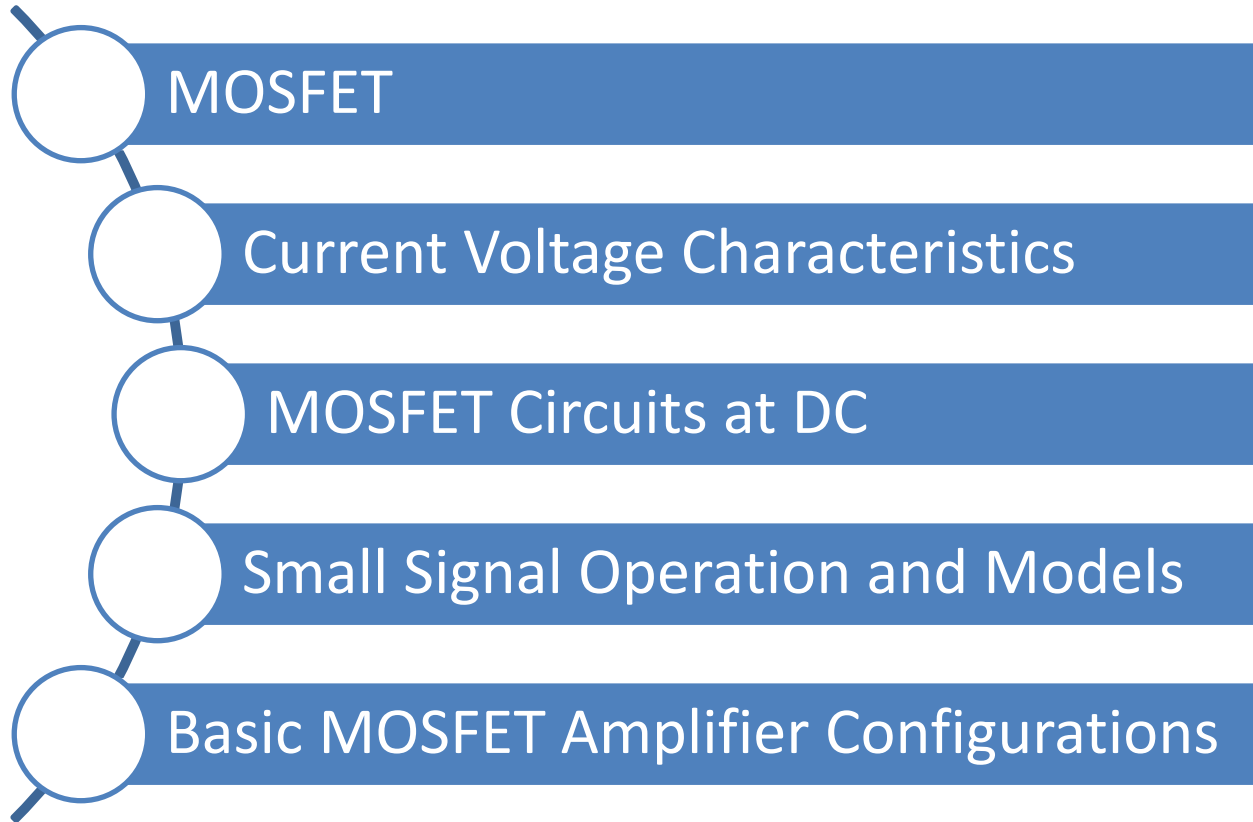


Electronic Circuits

Chapter 3: FET

Dr. Dung Trinh

Content



MOSFET

❖ **MOSFET**: **M**etal-**O**xide-**S**emiconductor **F**ield-**E**ffect **T**ransistor.



❖ According to the physics of the device, we can classify transistors into two main classes:

➤ **Field Effect Transistors (FET)**: Conduction is controlled by electric field which is produced by voltage applied to the control terminals. So, the control draws no current and FET is a voltage- controlled device.

➤ **Bipolar Junction Transistors (BJT)**: Diode-based device which is usually blocked unless the control terminals are forward- biased. So, the control is a current, and BJT is a current amplifier by nature.


MOSFET

  - ❖ **MOSFET** is a four-terminal device: gate (**G**), source (**S**), drain (**D**) and body (**B**).
- ❖ **Two kinds of MOSFETs**: n-channel (**NMOS**) and p-channel (**PMOS**) devices.
- ❖ The device structure is basically symmetric in terms of drain and source.
- ❖ Source and drain terminals are specified by the operation voltage.





MOSFET

- ❖ Gate voltage exceeds a threshold voltage $v_{GS} > V_t$: electrons start to accumulate on the substrate surface. $V_t = 0.3 \div 1 \text{ (V)}$
- ❖ The positive $v_{GS} > V_t$ is used to induce the channel and it is called **n-channel** enhancement type MOSFET.
- ❖ The induced n region *forms a channel for current flow from drain to source.*
- ❖ *The field controls the amount of charge* in the channel and determines the channel conductivity.

 

MOSFET – Small v_{DS}

  - ❖ **Small v_{DS} is applied:** free electrons travel from source to drain through the induced n-channel.
- ❖ The resulting current i_D flows from drain to source (opposite to the direction of the flow of negative charge).





- ❖ The resulting current i_D flows from drain to source (opposite to the direction of the flow of negative charge).
- ❖ The channel is controlled by the effective voltage or overdrive voltage:

$$V_{OV} = V_{GS} - V_t$$

MOSFET – Increasing v_{DS}

  - ❖ As v_{DS} is increased, the channel becomes more tapered and its resistance increases correspondingly.
- ❖ At the point $v_{DSsat} = v_{GS} - V_t$, the channel is pinched off at the drain side.
- ❖ Triode region: $v_{DS} < v_{DSsat}$
- ❖ Saturation region: $v_{DS} \geq v_{DSsat}$



MOSFET – IV Relationship

❖ Triode region: $i_D = k_n \left[(v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right]$

❖ Saturation region: $i_{Dsat} = \frac{1}{2} k_n (v_{GS} - V_t)^2$


❖ Channel resistance: $r_{DS} = \frac{1}{k_n (v_{GS} - V_t)}$

❖ Transconductance parameter: $k_n = \mu_n C_{ox} \frac{W}{L} = k'_n \frac{W}{L}$ where:

C_{ox} : oxide capacitance per unit area.


μ_n : mobility of electron in the inversion layer.

W and L : channel width and length.

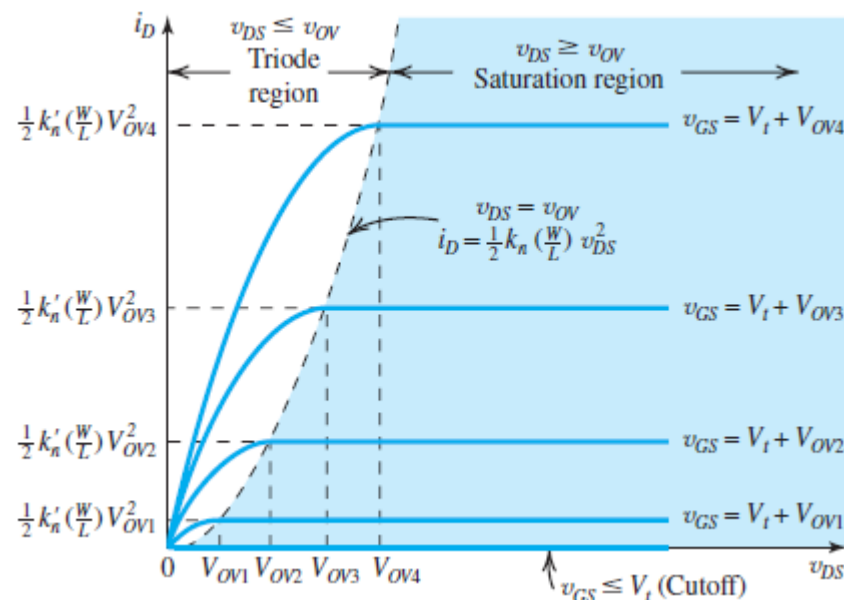


MOSFET – Circuit Symbols


❖ *n-channel enhancement-mode MOSFET:*

 


❖ *p-channel enhancement-mode MOSFET:*

 

NMOS – Current Voltage Characteristics

 

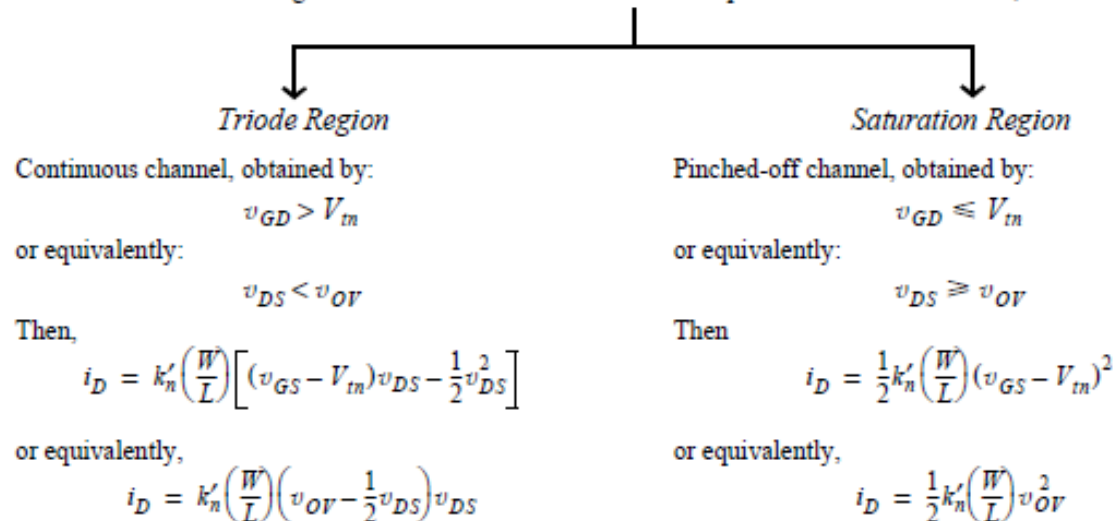- $v_{GS} < V_{tn}$: no channel; transistor in cut-off; $i_D = 0$
- $v_{GS} = V_{tn} + v_{OV}$: a channel is induced; transistor operates in the triode region or the saturation region depending on whether the channel is continuous or pinched-off at the drain end;



MOSFET - Current Voltage Characteristics


Example 1: Consider an NMOS transistor fabricated in a $L = 0.18\mu m$ process with $L = 0.18\mu m$ and $W = 2\mu m$. The process technology is specified to have $C_{ox} = 8.6 \text{ fF}/\mu m^2$, $\mu_n = 450 \text{ cm}^2/Vs$ and $V_{tn} = 0.5V$.

- Find V_{GS} and V_{DS} that result in the MOSFET operating at the edge of saturation with $I_D = 100\mu A$.
- If V_{GS} is kept constant, find V_{DS} that results in $I_D = 50\mu A$.
- To investigate the use of the MOSFET as a linear amplifier, let it be operating in saturation with $V_{DS} = 0.3V$. Find the change in i_D resulting from V_{GS} changing from $0.7V$ by $+0.01V$ and by $-0.01V$.

MOSFET – Finite Output Resistance

- ❖ In practice, increasing v_{DS} beyond v_{OV} does affect the channel somewhat.
- ❖ This effect can be accounted for i_D in the expression for by including a factor $(1 + \lambda v_{DS})$:

 
$$i_{Dsat} = \frac{1}{2} k_n (v_{GS} - V_t)^2 (1 + \lambda v_{DS})$$



- ❖ Defining the output resistance r_o as

$$r_o \equiv \left[\frac{\partial v_{DS}}{\partial i_D} \right]_{v_{GS}=const} = \frac{V_A}{I_D}$$

$$V_A = \frac{1}{\lambda}$$

 


MOSFET Circuits at DC

❖ DC analysis for MOSFET circuits:

- Assume the operation mode and solve the dc bias utilizing the corresponding current equation.
- Verify the assumption with terminal voltages (cutoff, triode and saturation).
- If the solution is invalid, change the assumption of operation mode and analyze again.

 
Example 2: The NMOS transistor in the following circuit has $V_t = 0.7V$, $\mu_n C_{ox} = 100\mu A/V^2$, $L = 1\mu m$ and $W = 32\mu m$. Design the circuit so that the transistor operates at $I_D = 0.4mA$ and $V_D = 0.5V$.




MOSFET Circuits at DC

Example 3: The NMOS transistor in the following circuit has $V_t = 0.6V$, $\mu_n C_{ox} = 200\mu A/V^2$, $L = 0.8\mu m$ and $W = 4\mu m$. Design the circuit so that the transistor operates at $I_D = 80\mu A$. Find the DC voltage V_D .

Example 4: Design the circuit so that the transistor operates at $V_D = 0.1V$. Let $V_t = 1V$, $k_n = 1mA/V^2$. Find the effective resistance between drain and source at this operating point.

 



Example 3

 

Example 4


MOSFET Circuits at DC

  Example 5: Determine the voltage and the current of all nodes and branches? $V_t = 1V$, $k_n = 1mA/V^2$.






MOSFET Circuits at DC

 Example 6: Design the following circuit so that the transistor operates in saturation with $I_D = 0.5\text{mA}$ and $V_D = 3\text{V}$. Let the enhancement-type PMOS transistor have $V_{tp} = -1\text{V}$ and $k'_p \frac{W}{L} = 1\text{mA/V}^2$. Assume $\lambda = 0$. What is the largest value that R_D can have while maintaining saturation-region operation?




MOSFET Circuits at DC

   Example 7: The NMOS and PMOS transistors in the following circuit are matched, with $k'_n \frac{W}{L} = k'_p \frac{W}{L} = 1 \text{ mA/V}^2$ and $V_{tn} = -V_{tp} = 1 \text{ V}$. Assume $\lambda = 0$ for both devices, find the drain currents i_{DN} and i_{DP} as well as the voltage v_o for $v_I = 0 \text{ V}, 2.5 \text{ V}$ and -2.5 V .



MOSFET in Amplifier Design

 


$$v_{DS} = V_{DD} - i_D R_D$$

❖ Input voltage increase \rightarrow drain current increase \rightarrow output voltage decrease.

$$v_{DS} = V_{DD} - \frac{1}{2} k_n R_D (v_{GS} - V_t)^2$$


MOSFET in Amplifier Design

 

- ❖ The signal to be amplified, $v_{gs}(t)$, a function of time t , is superimposed on the bias voltage. Thus the total instantaneous value of becomes:


$$v_{GS}(t) = V_{GS} + v_{gs}(t)$$

MOSFET in Amplifier Design

 

- ❖ The signal to be amplified, $v_{gs}(t)$, a function of time t , is superimposed on the bias voltage. Thus the total instantaneous value of becomes:

$$v_{GS}(t) = V_{GS} + v_{gs}(t)$$

 


$$A_v \equiv \frac{\partial v_{DS}}{\partial v_{GS}} \bigg|_{v_{GS}=V_{GS}} = -k_n(V_{GS} - V_t)R_D$$




MOSFET in Amplifier Design

 Example 8: The transistor is specified to have $V_t = 0.4V$, $k'_n = 0.4mA/V^2$, $W/L = 10$, $V_{DD} = 1.8V$, $R_D = 17.5k\Omega$, $V_{GS} = 0.6V$.

- For $v_{gs} = 0$, find V_{OV} , I_D , V_{DS} and A_v .
- What is the maximum symmetrical signal swing allowed at the drain? Hence find the maximum allowable amplitude of a sinusoidal v_{GS} .



MOSFET in Amplifier Design

   


$v_{DS} \approx 0$

Transistor as a switch

$I_D = 0$
 $v_{DS} = V_{DD}$

Small Signal Operation and Models

 

❖ The DC bias point:

$$I_D = \frac{1}{2} k_n (V_{GS} - V_t)^2 = \frac{1}{2} k_n V_{OV}^2$$

$$V_{DS} = V_{DD} - R_D I_D$$


❖ When the input signal v_{gs} applied

$$\begin{aligned} i_D &= \frac{1}{2} k_n (V_{GS} + v_{gs} - V_t)^2 \\ &= \frac{1}{2} k_n (V_{GS} - V_t)^2 + k_n (V_{GS} - V_t) v_{gs} + \frac{1}{2} k_n v_{gs}^2 \end{aligned}$$

❖ In order to reduce the non-linear distortion: $\frac{1}{2} k_n v_{gs}^2 \ll k_n (V_{GS} - V_t) v_{gs}$

$$\Leftrightarrow v_{gs} \ll 2(V_{GS} - V_t)$$

Small Signal Operation and Models

 

❖ If the small signal condition is satisfied:

$$i_D = \frac{1}{2} k_n (V_{GS} - V_t)^2 + k_n (V_{GS} - V_t) v_{gs} = I_D + i_d$$

❖ The MOSFET **transconductance** g_m :



$$g_m \equiv \frac{i_d}{v_{gs}} = k_n (V_{GS} - V_t)$$

❖ Voltage gain:


$$\begin{aligned} v_{DS} &= V_{DD} - i_D R_D = V_{DD} - (I_D + i_d) R_D \\ &= V_{DS} - i_d R_D \end{aligned}$$

$$A_v \equiv \frac{v_{ds}}{v_{gs}} = -g_m R_D$$

Small Signal Operation and Models

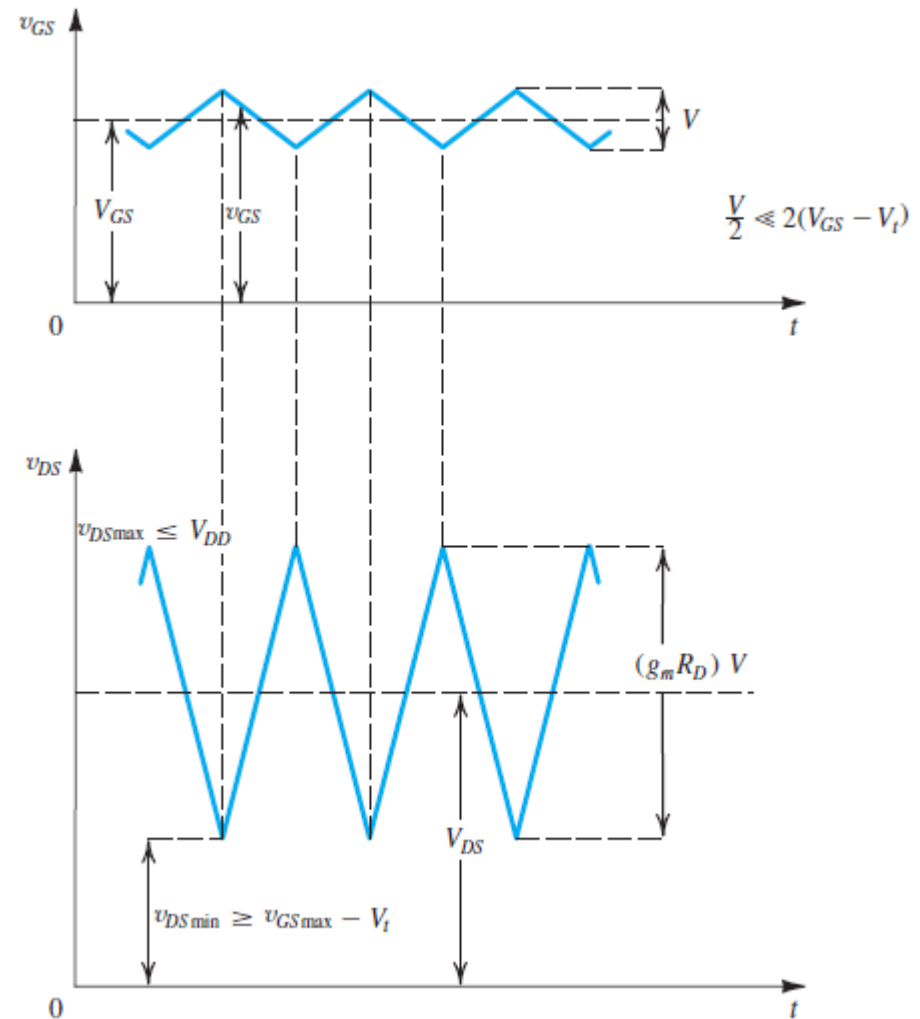 

Small Signal Model

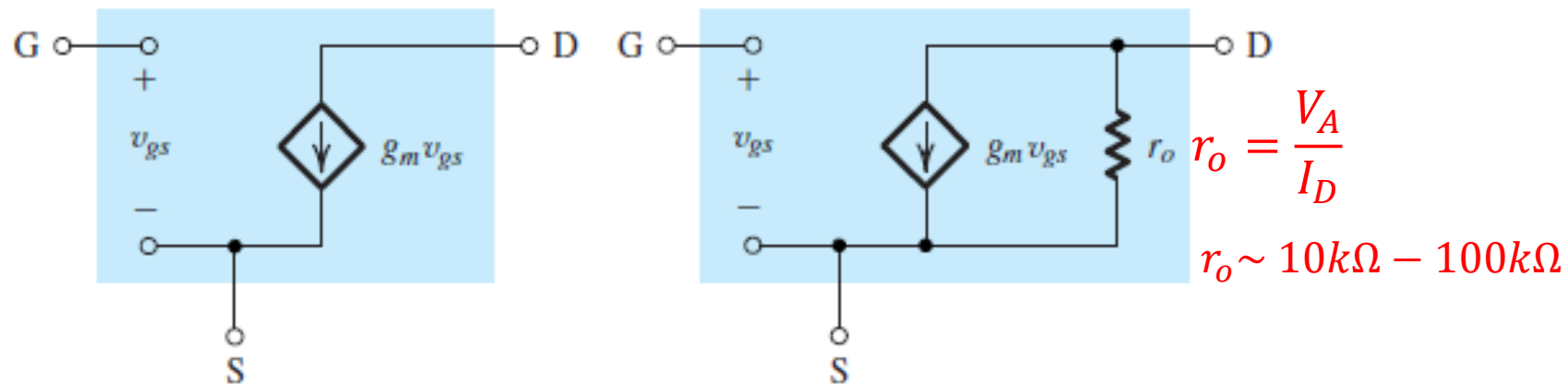


- ❖ The current I_D is the value of the dc drain current:


$$I_D = \frac{1}{2} k_n (V_{GS} - V_t)^2 = \frac{1}{2} k_n V_{OV}^2$$

- ❖ The trans-conductance g_m :
 
$$g_m = k_n V_{OV} = k'_n (W/L) V_{OV} = \frac{2I_D}{V_{OV}}$$




Small Signal Model – T model

 

Small Signal Model

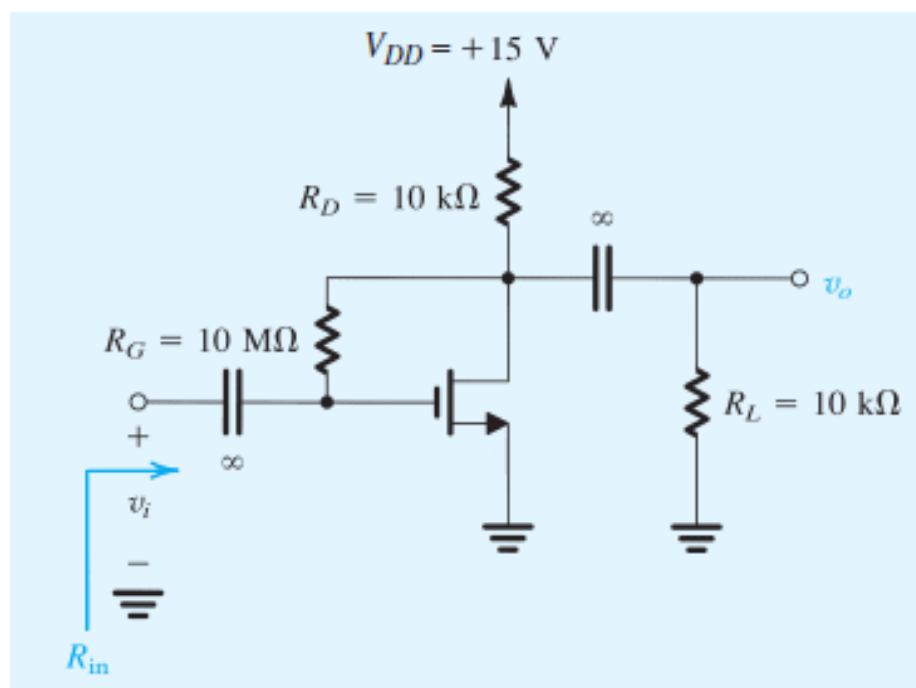Example 9: A discrete common-source MOSFET amplifier utilizing a drain-to-gate resistance R_G for biasing purposes. The transistor has $V_t = 1.5\text{ V}$, $k'_n W/L = 0.25\text{ mA/V}^2$ and $V_A = 50\text{ V}$. Determine its small-signal voltage gain and its input resistance.



Summary

Small-Signal Parameters

NMOS transistors

■ Transconductance:

$$g_m = \mu_n C_{ox} \frac{W}{L} V_{OV} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = \frac{2I_D}{V_{OV}}$$


■ Output resistance:

$$r_o = V_A / I_D = 1 / \lambda I_D$$


PMOS transistors

Same formulas as for NMOS *except* using $|V_{OV}|$, $|V_A|$, and replacing μ_n with μ_p .


Small-Signal Equivalent Circuit Models

 


Hybrid- π model

 


T models

 


The Three Basic Configurations

 

(a) Common Source (CS)

 



(b) Common Gate (CG)

 

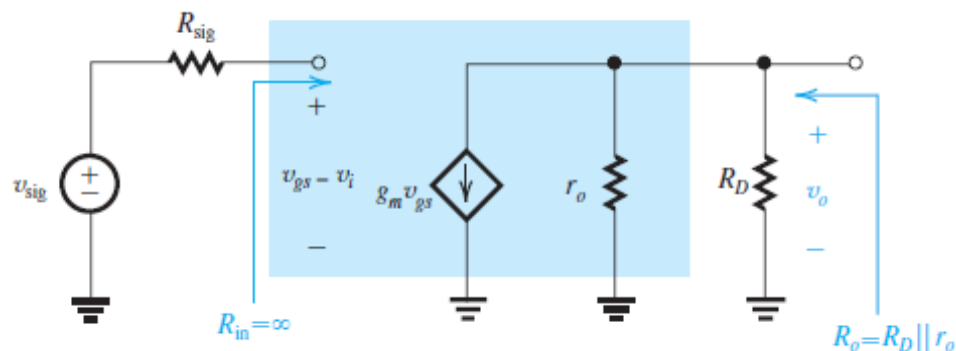 (c) Common Drain (CD)

Common Source Amplifier

- ❖ The common source is the **most widely used**.
- ❖ The bulk of the voltage gain is obtained by using one or more **Common Source stages in the cascade**.



Characteristic Parameters of the CS Amplifier:

- Open circuit voltage gain:

$$A_{v0} = -g_m(R_D \parallel r_o) \approx -g_m R_D$$

- Overall voltage gain:

$$G_v = -g_m(R_D \parallel r_o \parallel R_L)$$

- Input resistance:



$$R_{in} = \infty$$

- Output resistance:

$$R_{out} = R_D \parallel r_o \approx R_D$$

Common Source Amplifier

  - ❖ The common source is the **most widely used**.
- ❖ The bulk of the voltage gain is obtained by using one or more **Common Source stages in the cascade**.



Characteristic Parameters of the CS Amplifier:

- Open circuit voltage gain:

$$A_v = -g_m(R_D \parallel r_o) \approx -g_m R_D$$

- Overall voltage gain:

$$G_v = -g_m(R_D \parallel r_o \parallel R_L)$$


- Input resistance:

$$R_{in} = \infty$$

- Output resistance:

$$R_{out} = R_D \parallel r_o \approx R_D$$

Common Source Amplifier

 

CS amplifier with source resistance

Characteristic Parameters of the CS Amplifier
(with source resistance):

$$i = \frac{v_i}{1/g_m + R_s} = \frac{g_m}{1 + g_m R} v_i$$

$$v_o = -i R_D$$

- Open circuit voltage gain:


$$A_v = \frac{v_o}{v_i} = - \frac{g_m R_D}{1 + g_m R_S}$$

- Input resistance:

$$R_{in} = \infty$$


- Output resistance:
 
$$R_{out} = R_D \parallel r_o \approx R_D$$



Common Gate Amplifier

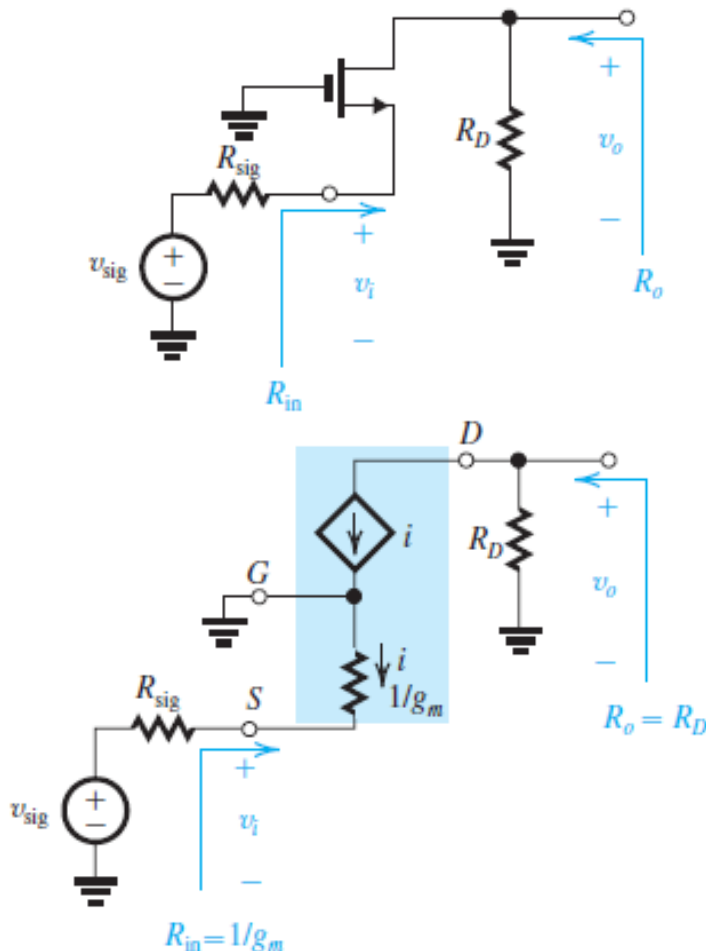❖ Common Gate amplifier is used to obtain **wide bandwidth**.



Characteristic Parameters of the CS Amplifier:

- Open circuit voltage gain:

$$A_v = g_m R_D$$

- Overall voltage gain:

$$G_v = \frac{R_D \parallel R_L}{R_{sig} + 1/g_m}$$

- Input resistance:

$$R_{in} = \frac{1}{g_m} \quad \text{Disadvantage!!!}$$


- Output resistance:

$$R_{out} = R_D$$

Common Drain Amplifier (Source Follower)



The need for voltage buffers: the amplifier has

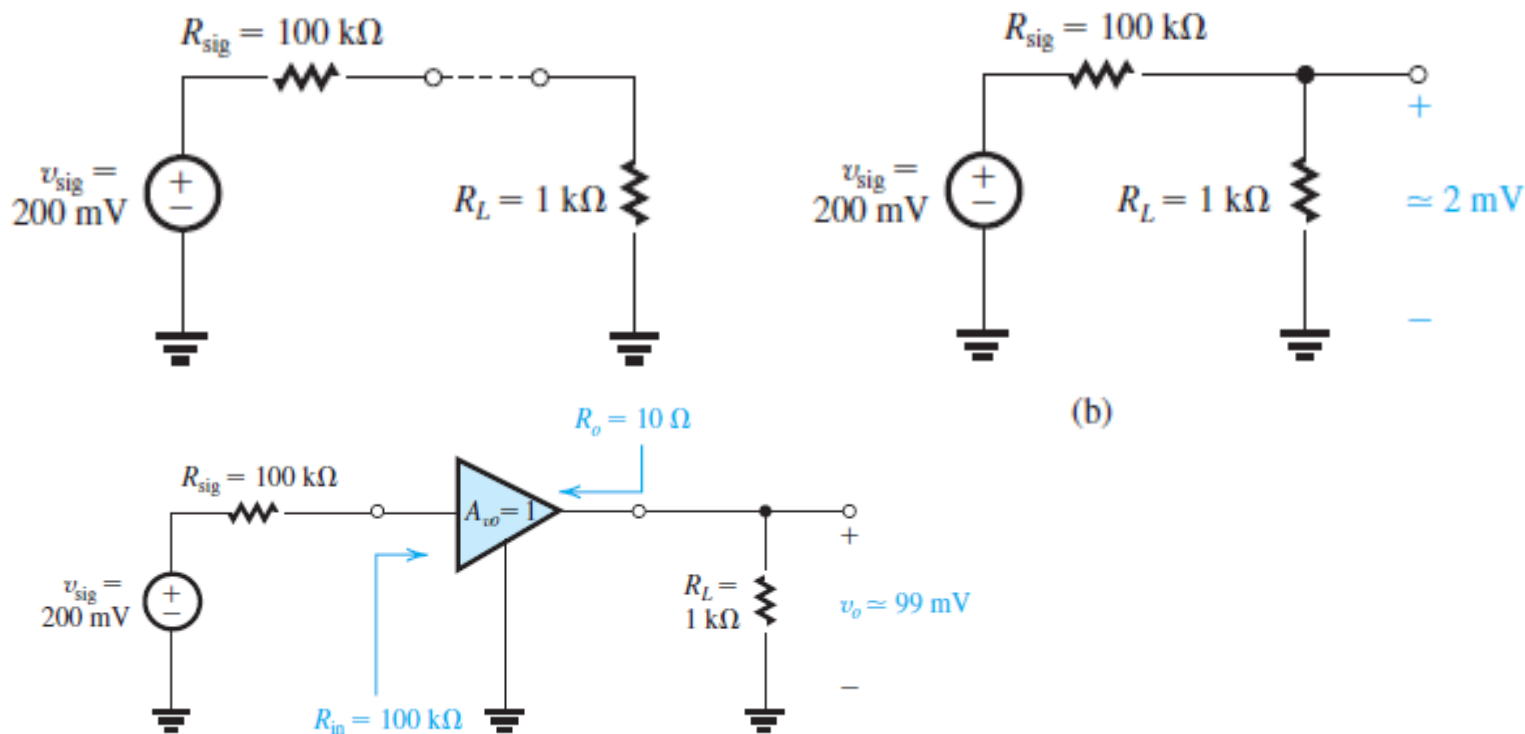- High input resistance.
- Low output resistance.



Common Drain Amplifier (Source Follower)

 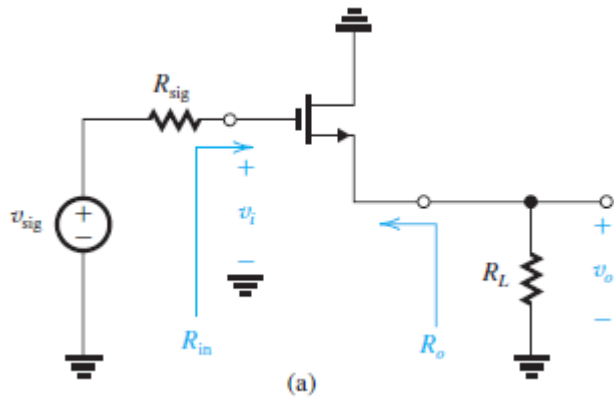❖ Common Drain amplifier is usually used as a voltage buffer.



Characteristic Parameters of the CS Amplifier:

- Open circuit voltage gain:

$$A_v = \frac{R_L}{R_L + 1/g_m} \approx 1$$

- Overall voltage gain:

$$G_v = \frac{R_L}{R_L + 1/g_m} \approx 1$$


- Input resistance:

$$R_{in} = \infty$$

- Output resistance:


$$R_{out} = 1/g_m$$

Discrete Circuit MOS Amplifiers

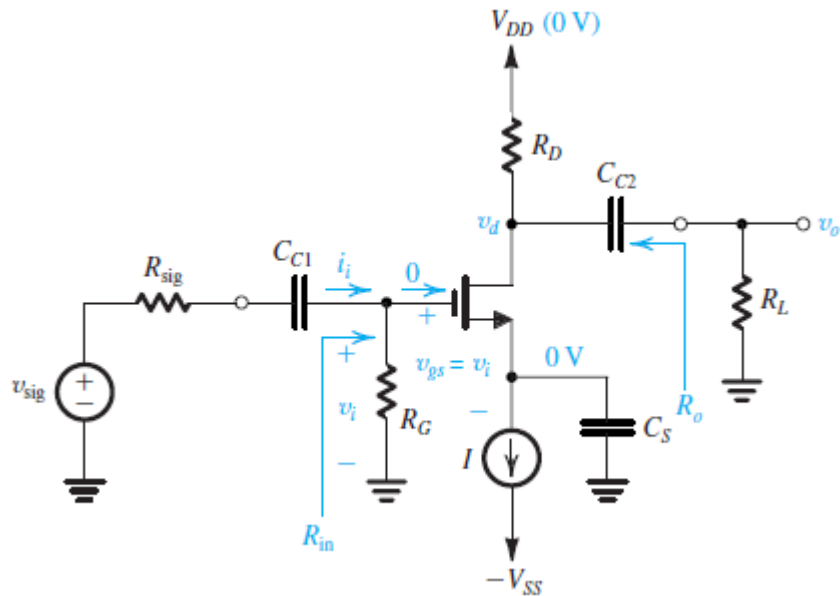


 Example 9: Given $V_{DD} = V_{SS} = 10V$, $k_n = 1mA/V^2$, $I = 0.5mA$, $R_D = 15k\Omega$, $R_G = 4.7M\Omega$, $V_t = 1.5V$, $V_A = 75V$.

Calculate input, output resistance and overall voltage gain. $R_{sig} = 100k\Omega$, $R_L = 15k\Omega$.




Discrete Circuit MOS Amplifiers

 


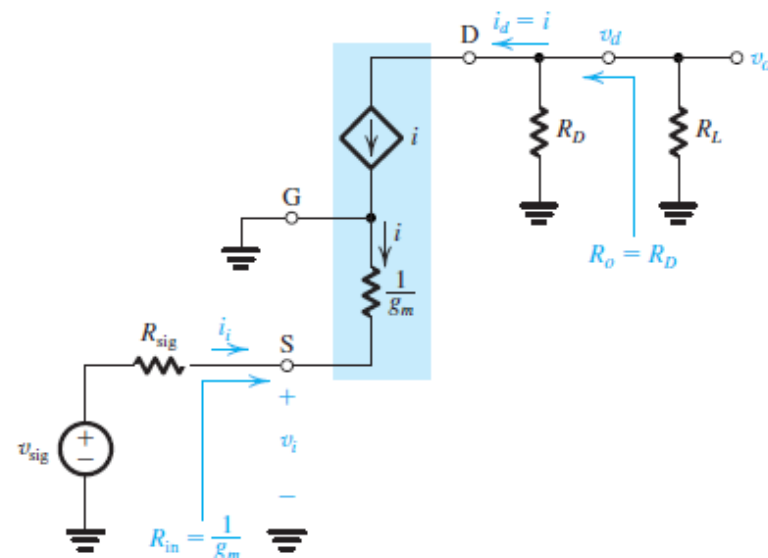Example 10: Given $V_{DD} = V_{SS} = 10V$, $k_n = 1mA/V^2$, $I = 0.5mA$, $R_D = 15k\Omega$, $R_G = 4.7M\Omega$, $V_t = 1.5V$, $g_m = 1mA/V$.

Calculate input, output resistance and overall voltage gain. $R_{sig} = 50\Omega$, $R_L = 15k\Omega$.




Discrete Circuit MOS Amplifiers

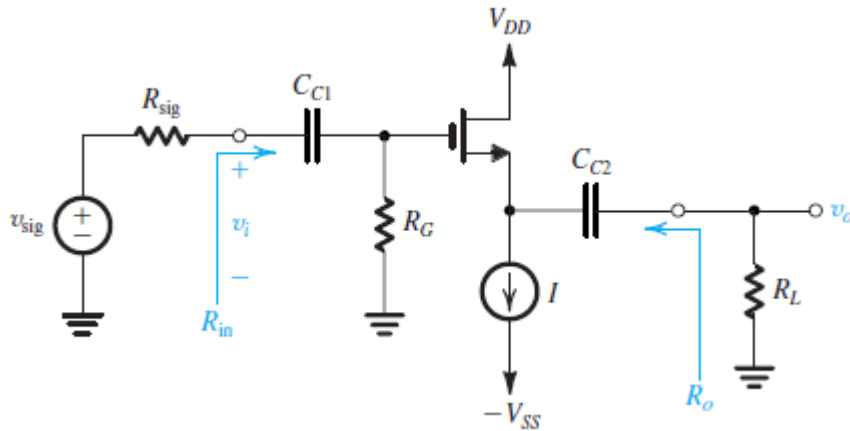

 Example 11: Given $V_{DD} = V_{SS} = 10V$, $k_n = 1mA/V^2$, $I = 0.5mA$, $R_D = 15k\Omega$, $R_G = 4.7M\Omega$, $V_t = 1.5V$, $g_m = 1mA/V$.

Calculate input, output resistance and overall voltage gain. $R_{sig} = 1M\Omega$, $R_L = 15k\Omega$.



Summary

Amplifier type	Characteristics ^{a, b}				
	R_{in}	A_{vo}	R_o	A_v	G_v
Common source	∞	$-\mathcal{G}_m R_D$	R_D	$-\mathcal{G}_m (R_D \parallel R_L)$	$-\mathcal{G}_m (R_D \parallel R_L)$
Common source with R_s	∞	$-\frac{\mathcal{G}_m R_D}{1 + \mathcal{G}_m R_s}$	R_D	$-\frac{\mathcal{G}_m (R_D \parallel R_L)}{1 + \mathcal{G}_m R_s}$	$-\frac{\mathcal{G}_m (R_D \parallel R_L)}{1 + \mathcal{G}_m R_s}$
				$-\frac{R_D \parallel R_L}{1/\mathcal{G}_m + R_s}$	$-\frac{R_D \parallel R_L}{1/\mathcal{G}_m + R_s}$
Common gate	$\frac{1}{\mathcal{G}_m}$	$\mathcal{G}_m R_D$	R_D	$\mathcal{G}_m (R_D \parallel R_L)$	$\frac{R_D \parallel R_L}{R_{sig} + 1/\mathcal{G}_m}$
Source follower	∞	1	$\frac{1}{\mathcal{G}_m}$	$\frac{R_L}{R_L + 1/\mathcal{G}_m}$	$\frac{R_L}{R_L + 1/\mathcal{G}_m}$

Q&A